

# Lecture 17: Lattice Structures

## Foundations of Digital Signal Processing

### Outline

- Implementation of FIR Filters
- Implementation of IIR Filters
- Implementation of Lattice Filters

## ■ Homework #7

- Due today
- Submit via canvas

## ■ Coding Problem #4

- Due today
- Submit via canvas

## ■ In 1.5 weeks

- Exam #2 (yay!)

# Lecture 17: Lattice Structures

Foundations of Digital Signal Processing

## Outline

- **Implementation of FIR Filters**
- Implementation of IIR Filters
- Implementation of Lattice Filters

# Implementing FIR Filters


## ■ FIR Direct Form

$$y[n] = \sum_{m=0}^{M-1} h[m]x[n-m]$$

# Implementing FIR Filters

## ■ FIR Direct Form ( $M = 1$ )


$$y[n] = h[0] + h[1]x[n - 1]$$

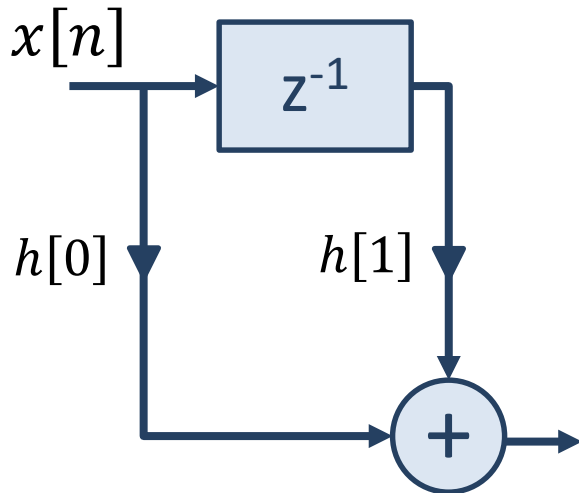

# Implementing FIR Filters

## ■ FIR Direct Form


$$y[n] = \sum_{m=0}^{M-1} h[m]x[n-m]$$

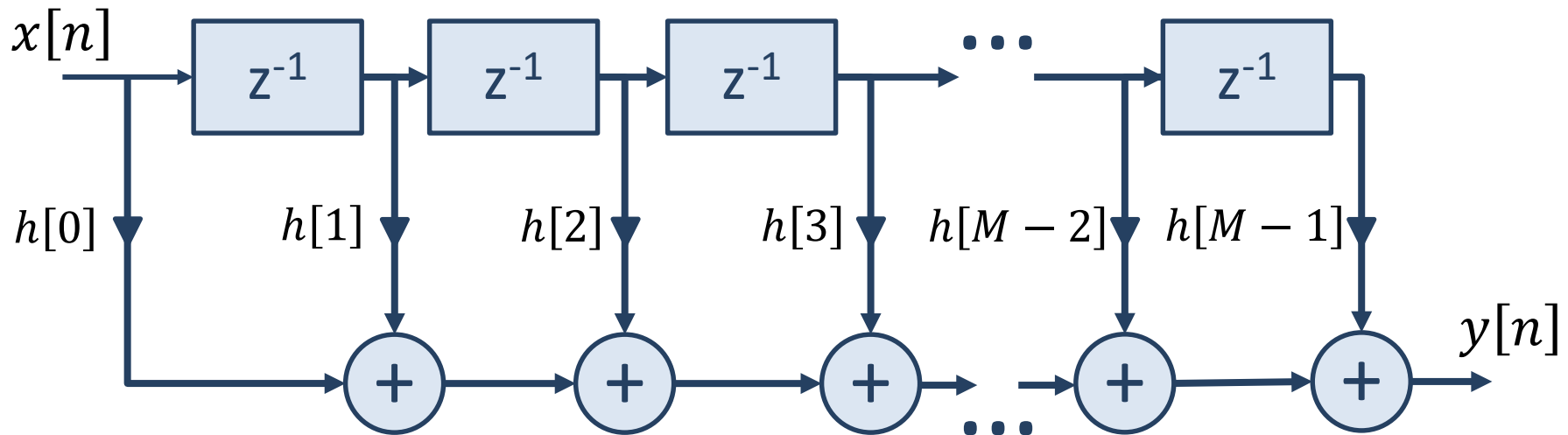

# Implementing FIR Filters
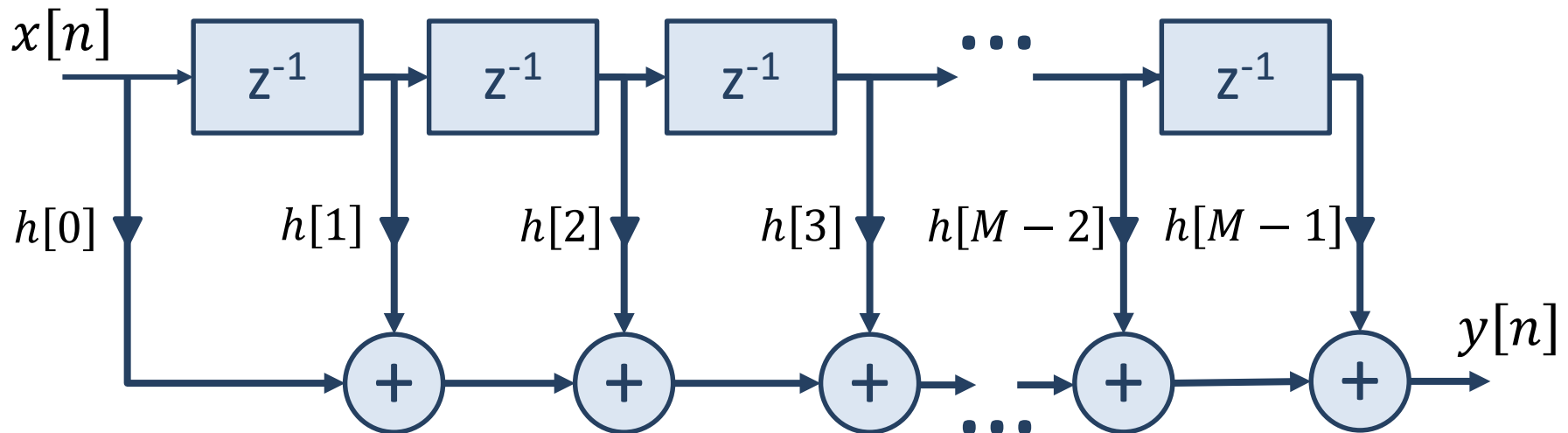
## ■ FIR Direct Form


- What are some benefits of using a direct form implementation?



# Implementing FIR Filters
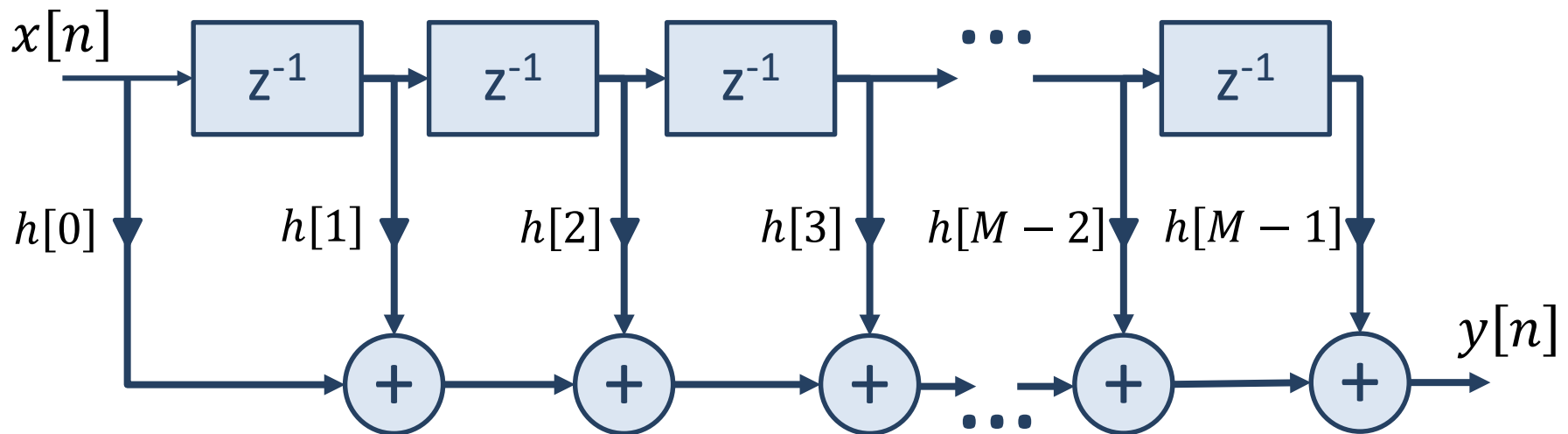
## ■ FIR Direct Form

- If the impulse is symmetric, then we can shorten this






# Implementing FIR Filters
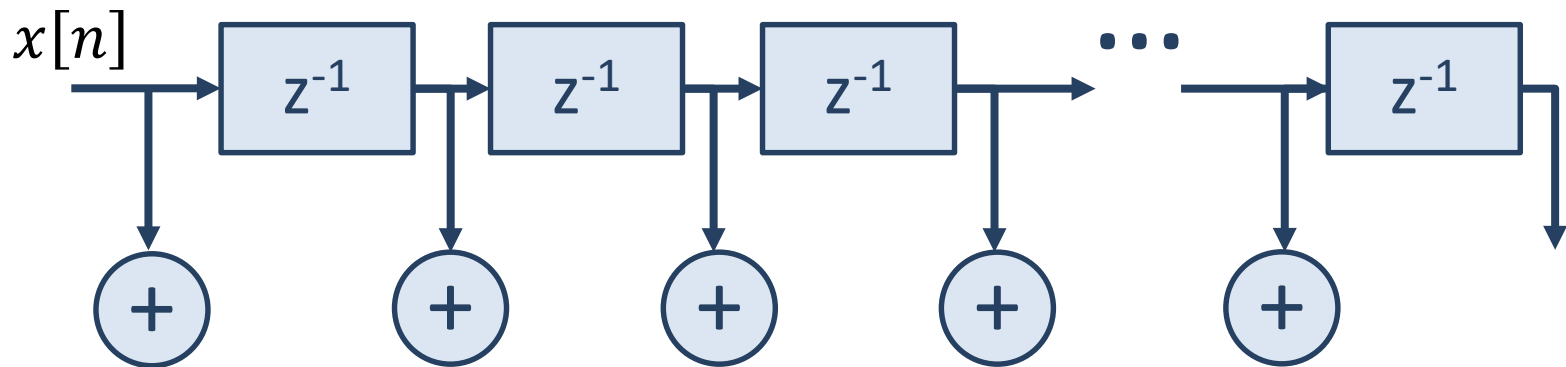
## ■ FIR Direct Form


- If the impulse is symmetric, then we can shorten this



# Implementing FIR Filters
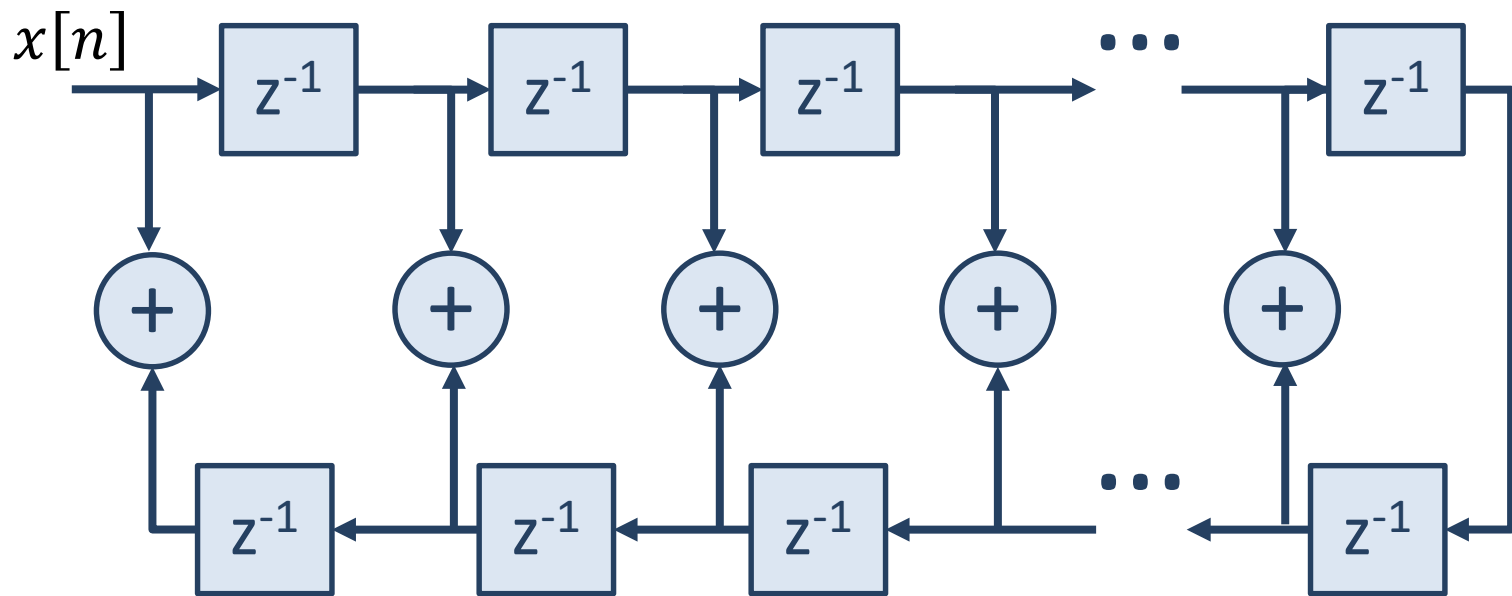
## ■ FIR Direct Form


- If the impulse is symmetric, then we can shorten this



# Implementing FIR Filters
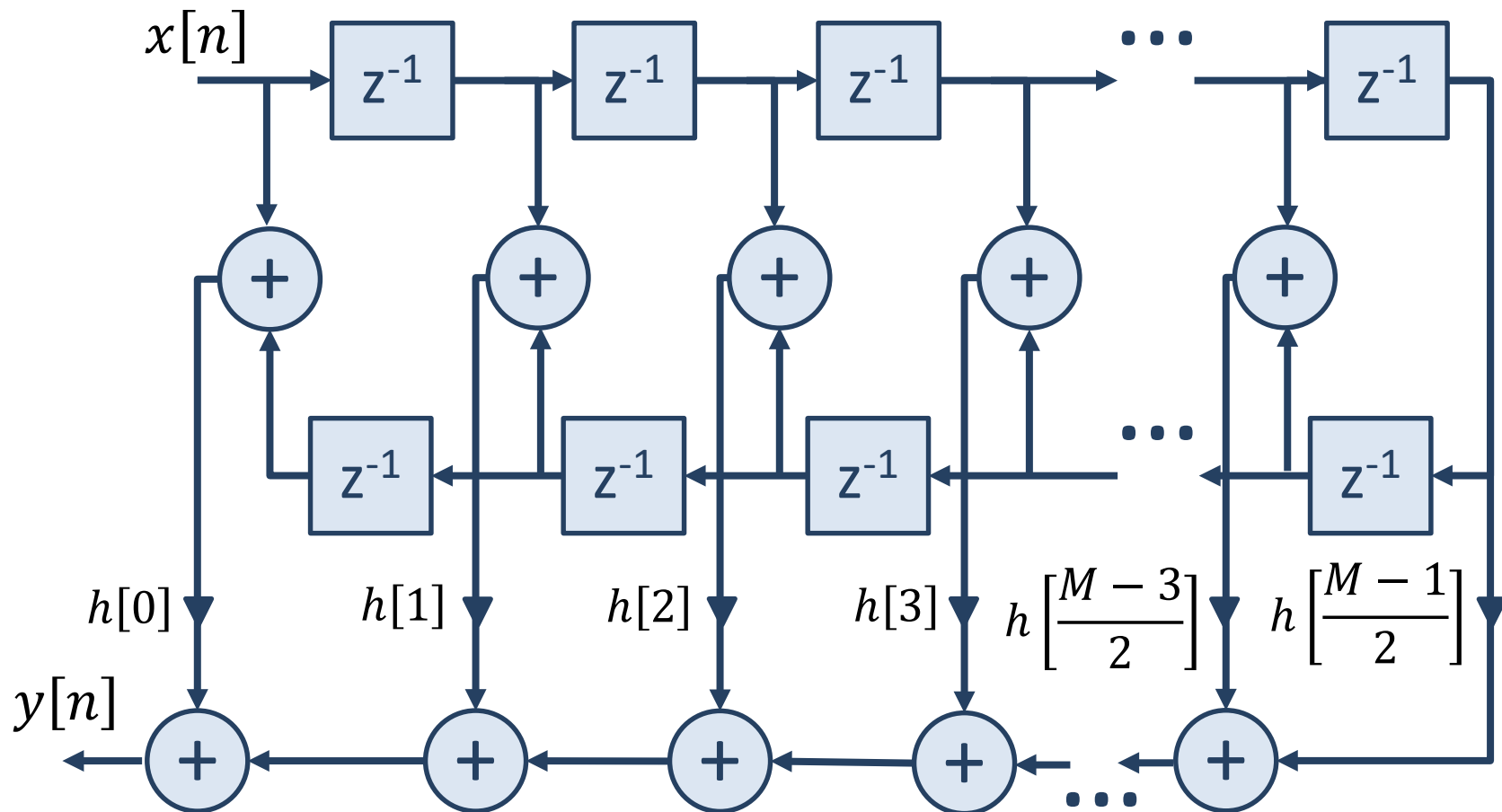
## ■ FIR Direct Form


- If the impulse is symmetric, then we can shorten this



# Implementing FIR Filters
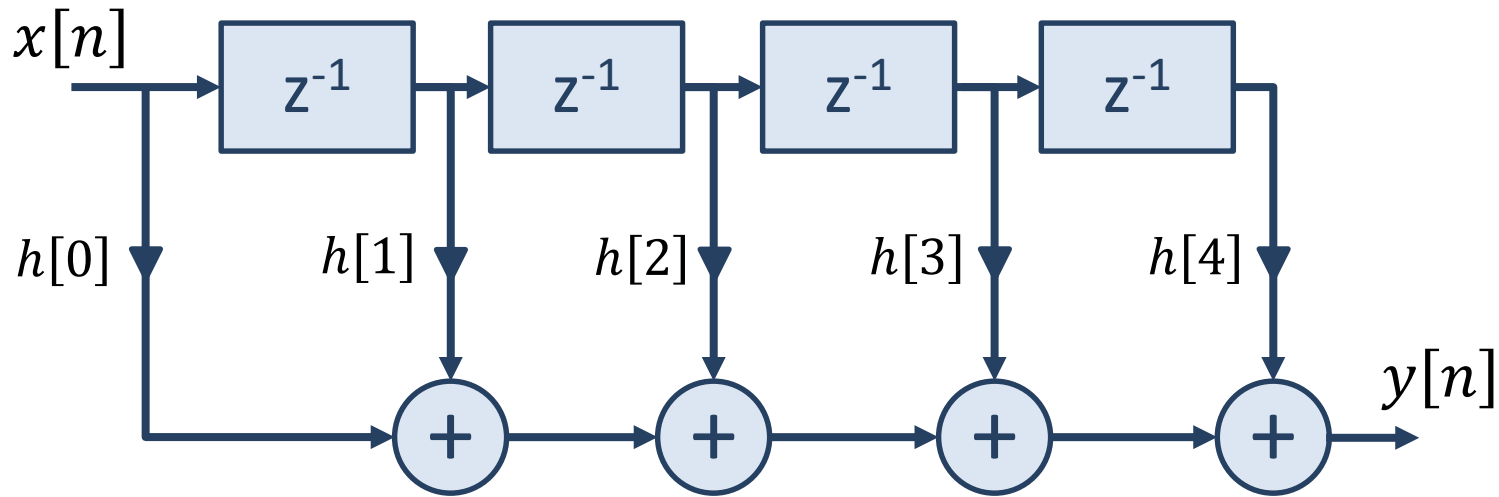
## ■ FIR Direct Form


- Non-symmetric impulse response (4 multiplications)



# Implementing FIR Filters
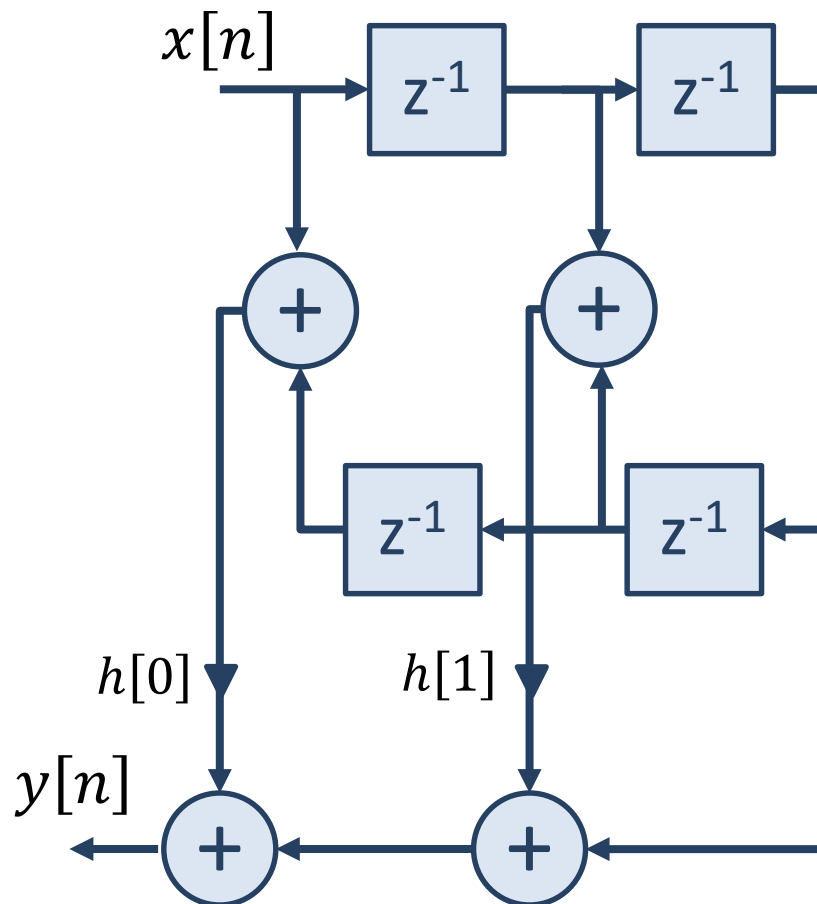
## ■ FIR Direct Form


- Symmetric impulse response (2 multiplications)



# Implementing FIR Filters
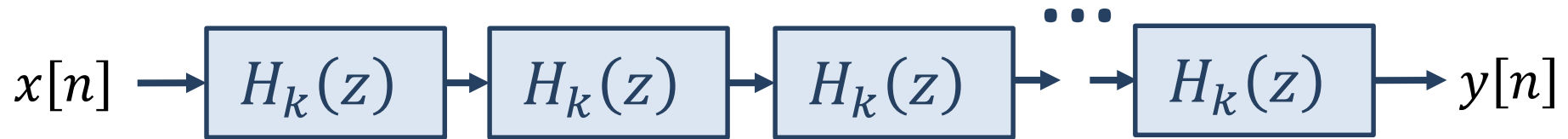
## ■ FIR Cascade Form



$$Y[z] = X(z) \sum_{m=0}^{M-1} h[m]z^{-m} = X(z) \prod_{k=1}^K H_k(z)$$



# Implementing FIR Filters
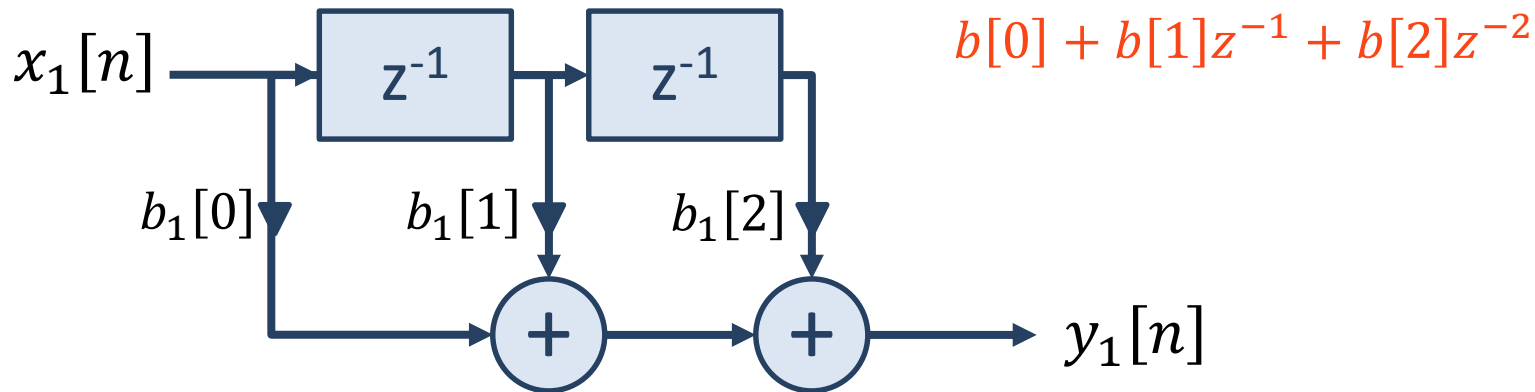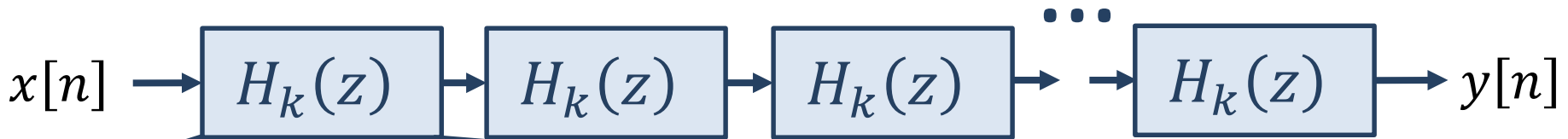
## ■ FIR Cascade Form



$$Y[z] = X(z) \sum_{m=0}^{M-1} h[m]z^{-m} = X(z) \prod_{k=1}^K H_k(z)$$



# Implementing FIR Filters
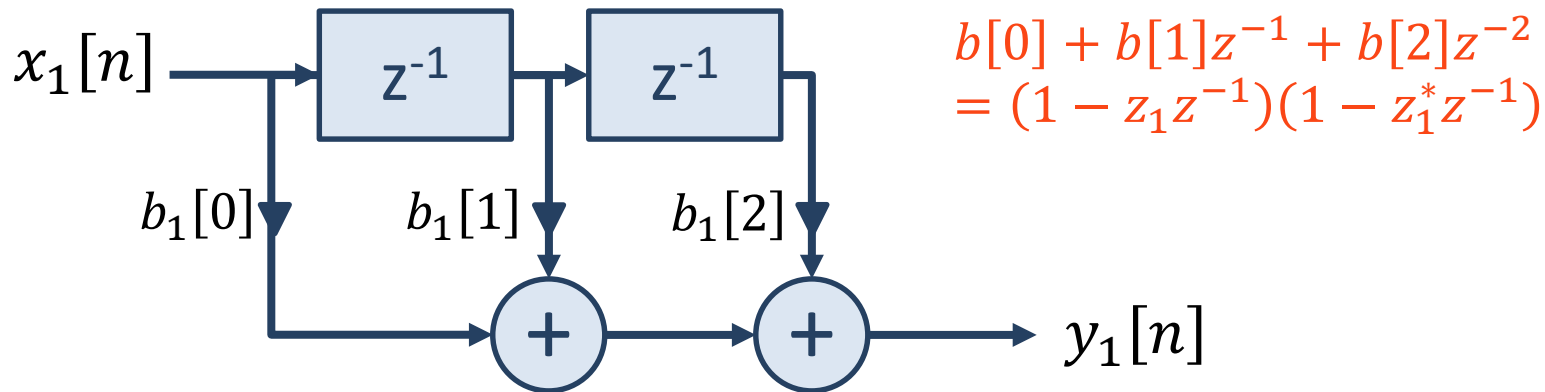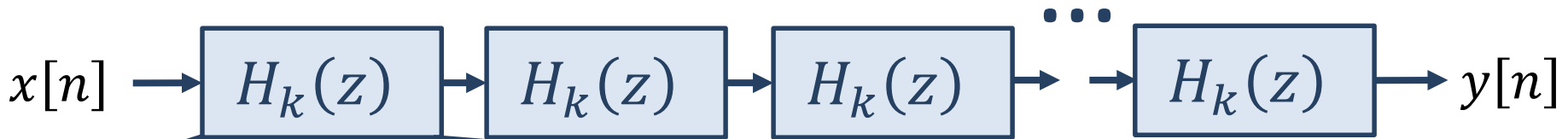
## ■ FIR Cascade Form

$$Y[z] = X(z) \sum_{m=0}^{M-1} h[m]z^{-m} = X(z) \prod_{k=1}^K H_k(z)$$







# Implementing FIR Filters
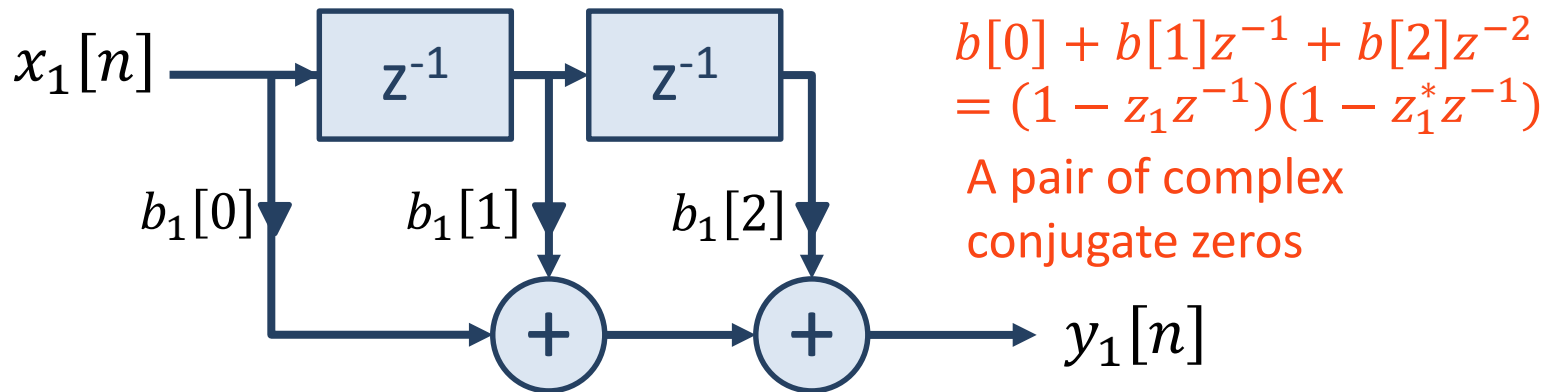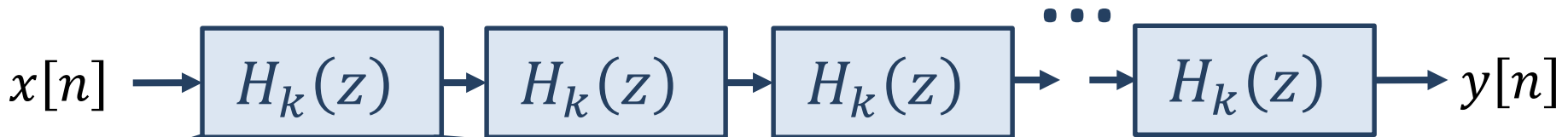
## ■ FIR Cascade Form


$$Y[z] = X(z) \sum_{m=0}^{M-1} h[m]z^{-m} = X(z) \prod_{k=1}^K H_k(z)$$



# Implementing FIR Filters
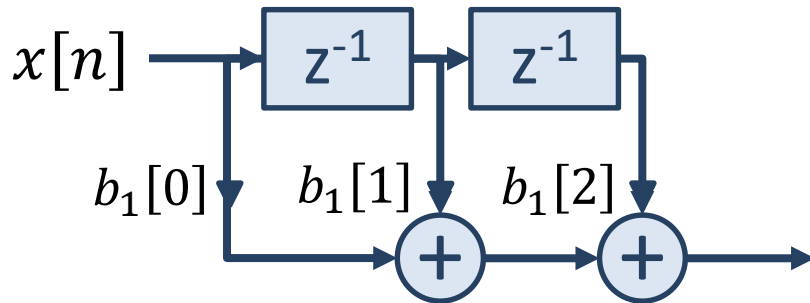
## ■ FIR Cascade Form


- What are some benefits of using a cascade form implementation?



# Implementing FIR Filters
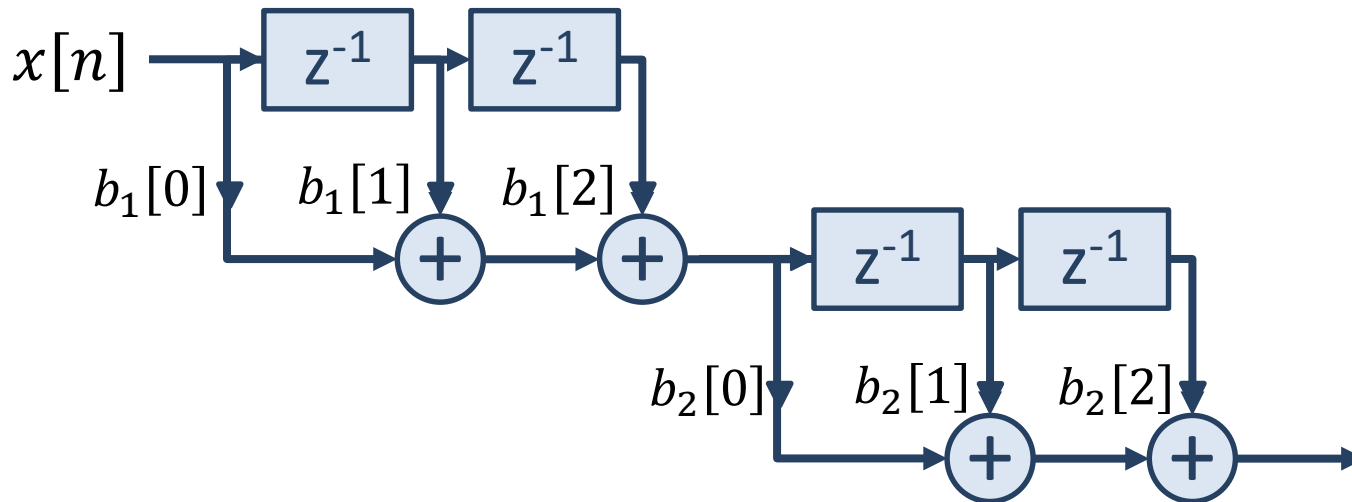
## ■ FIR Cascade Form


- What are some benefits of using a cascade form implementation?



# Implementing FIR Filters
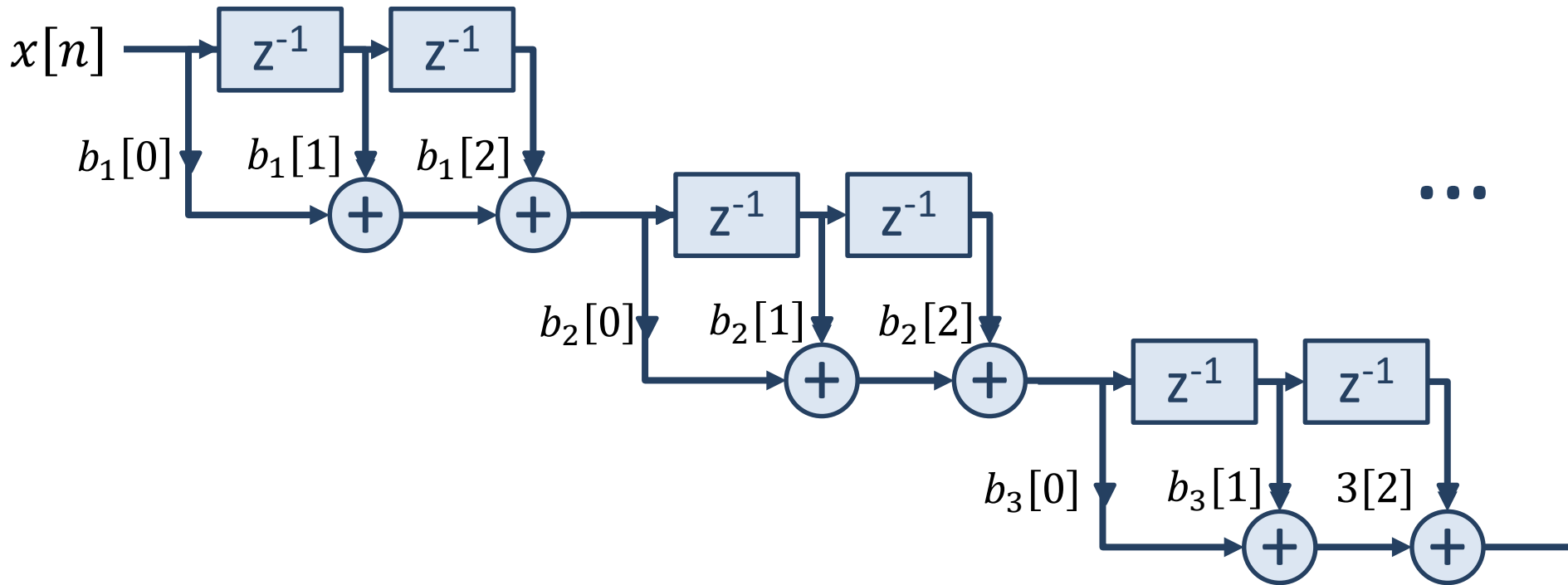
## ■ FIR Cascade Form


- What are some benefits of using a cascade form implementation?



# Implementing FIR Filters
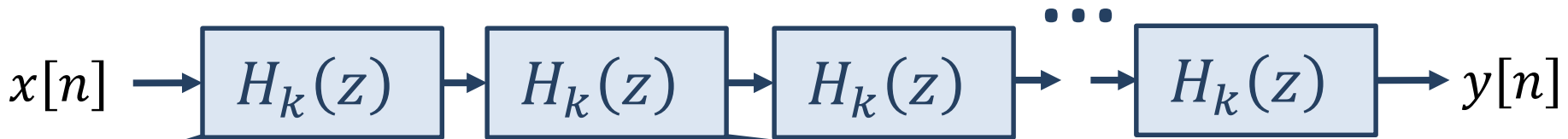
## ■ FIR Cascade Form (if the impulse response is symmetric)

$$Y[z] = X(z) \sum_{m=0}^{M-1} h[m]z^{-m} = X(z) \prod_{k=1}^K H_k(z)$$





$$(1 - z_1 z^{-1})(1 - z_1^* z^{-1}) \\ \left(1 - \frac{1}{z_1} z^{-1}\right) \left(1 - \frac{1}{z_1^*} z^{-1}\right)$$

# Implementing FIR Filters
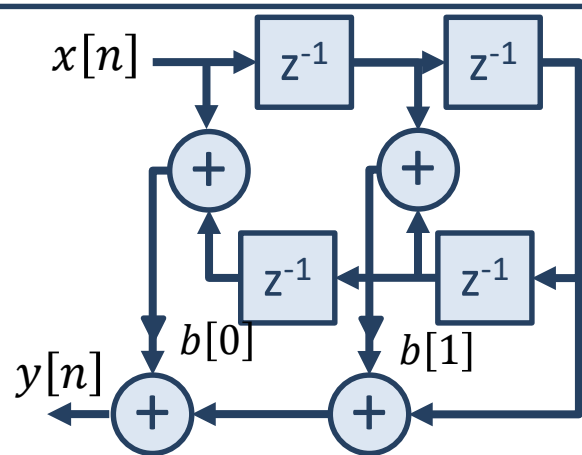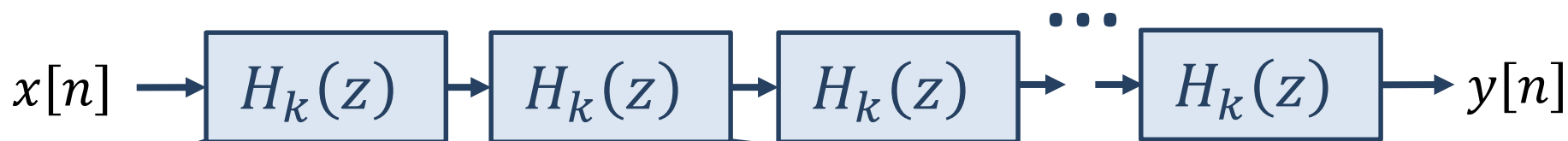
## ■ FIR Cascade Form (if the impulse response is symmetric)

$$Y[z] = X(z) \sum_{m=0}^{M-1} h[m]z^{-m} = X(z) \prod_{k=1}^K H_k(z)$$




$$(1 - z_1 z^{-1})(1 - z_1^* z^{-1})$$
$$\left(1 - \frac{1}{z_1} z^{-1}\right) \left(1 - \frac{1}{z_1^*} z^{-1}\right)$$

# Implementing FIR Filters
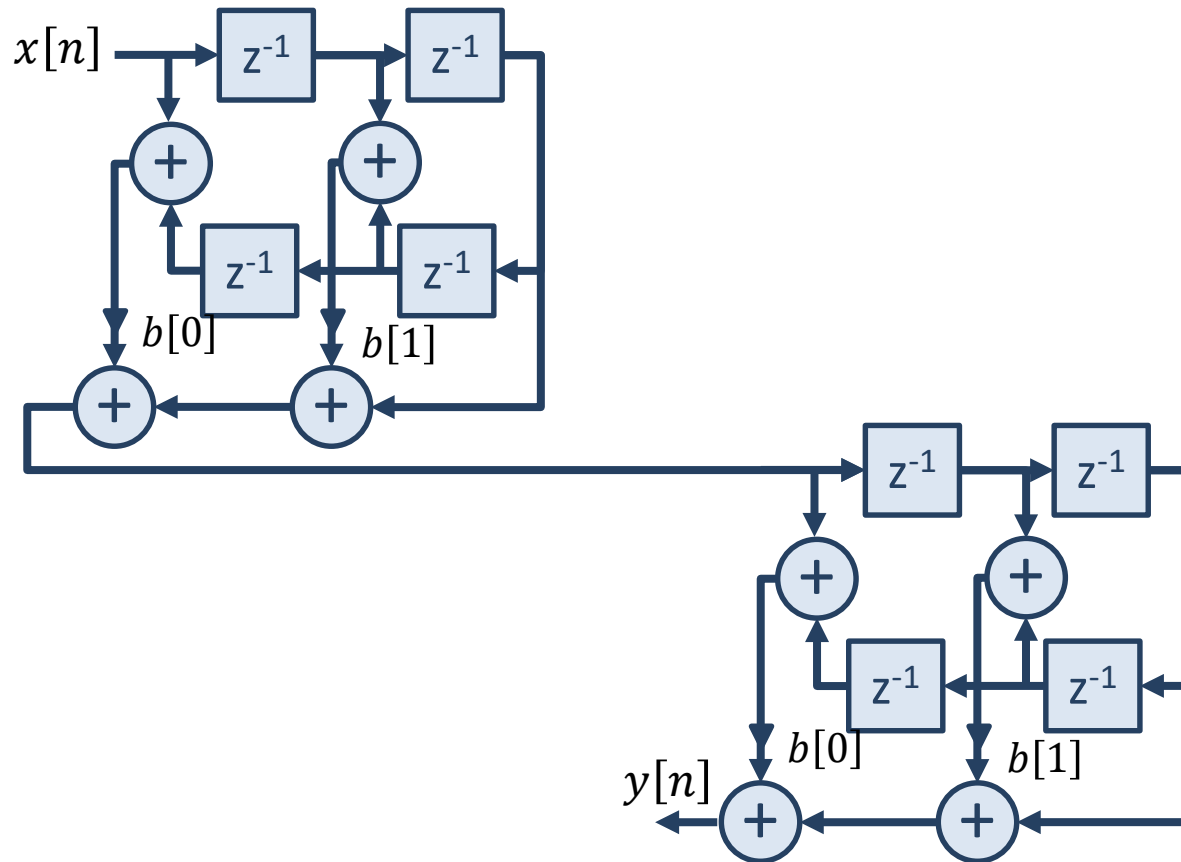
## ■ FIR Cascade Form

- What are some benefits of using a cascade form implementation?



...

# Implementing FIR Filters

## ■ Frequency Sampling Form

$$H[k] = \sum_{n=0}^{N-1} h[n] e^{-j\frac{2\pi}{N}kn} \quad , \quad h[n] = \frac{1}{N} \sum_{k=0}^{N-1} H[k] e^{j\frac{2\pi}{N}kn}$$



# Implementing FIR Filters

## ■ Frequency Sampling Form

$$H[k] = \sum_{n=0}^{N-1} h[n] e^{-j\frac{2\pi}{N}kn} \quad , \quad h[n] = \frac{1}{N} \sum_{k=0}^{N-1} H[k] e^{j\frac{2\pi}{N}kn}$$

$$\begin{aligned} H(z) &= \sum_{n=0}^{N-1} h[n] z^{-n} = \sum_{n=0}^{N-1} \left( \frac{1}{N} \sum_{k=0}^{N-1} H[k] e^{j\frac{2\pi}{N}kn} \right) z^{-n} \\ &= \sum_{n=0}^{N-1} \left( \frac{1}{N} \sum_{k=0}^{N-1} H[k] e^{j\frac{2\pi}{N}kn} \right) z^{-n} \\ &= \sum_{k=0}^{N-1} \left( H[k] \frac{1}{N} \sum_{n=0}^{N-1} e^{j\frac{2\pi}{N}kn} z^{-n} \right) \end{aligned}$$

# Implementing FIR Filters

## ■ Frequency Sampling Form

$$H[k] = \sum_{n=0}^{N-1} h[n] e^{-j\frac{2\pi}{N}kn} \quad , \quad h[n] = \frac{1}{N} \sum_{k=0}^{N-1} H[k] e^{j\frac{2\pi}{N}kn}$$

$$\begin{aligned} H(z) &= \sum_{n=0}^{N-1} h[n] z^{-n} = \sum_{n=0}^{N-1} \left( \frac{1}{N} \sum_{k=0}^{N-1} H[k] e^{j\frac{2\pi}{N}kn} \right) z^{-n} \\ &= \sum_{k=0}^{N-1} \left( H[k] \frac{1}{N} \frac{1 - e^{j\frac{2\pi}{N}kN} z^{-N}}{1 - e^{j\frac{2\pi}{N}kn} z^{-n}} \right) \\ &= \frac{1 - e^{j\frac{2\pi}{N}kN} z^{-N}}{N} \sum_{k=0}^{N-1} \left( \frac{H[k]}{1 - e^{j\frac{2\pi}{N}kn} z^{-n}} \right) \end{aligned}$$

# Implementing FIR Filters

## ■ Frequency Sampling Form

$$H(z) = \frac{1 - e^{j\frac{2\pi}{N}kN} z^{-N}}{N} \sum_{k=0}^{N-1} \left( \frac{H[k]}{1 - e^{j\frac{2\pi}{N}kn} z^{-n}} \right)$$

# Implementing FIR Filters


## ■ Frequency Sampling Form

$$H(z) = \underbrace{\frac{1 - e^{j\frac{2\pi}{N}kN} z^{-N}}{N}}_{\text{FIR Filter}} \sum_{k=0}^{N-1} \left( \overbrace{\frac{H[k]}{1 - e^{j\frac{2\pi}{N}kn} z^{-n}}}^{\text{Weights}} \right) \underbrace{\phantom{\frac{H[k]}{1 - e^{j\frac{2\pi}{N}kn} z^{-n}}}}_{\text{IIR Filter}}$$

# Implementing FIR Filters

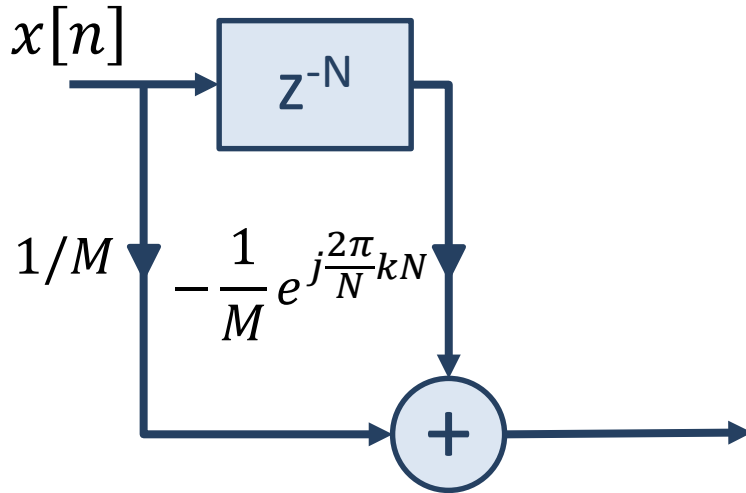
## ■ Frequency Sampling Form

$$H(z) = \underbrace{\frac{1 - e^{j\frac{2\pi}{N}kN} z^{-N}}{N}} \sum_{k=0}^{N-1} \left( \frac{H[k]}{1 - e^{j\frac{2\pi}{N}kn} z^{-n}} \right)$$



# Implementing FIR Filters


## ■ Frequency Sampling Form

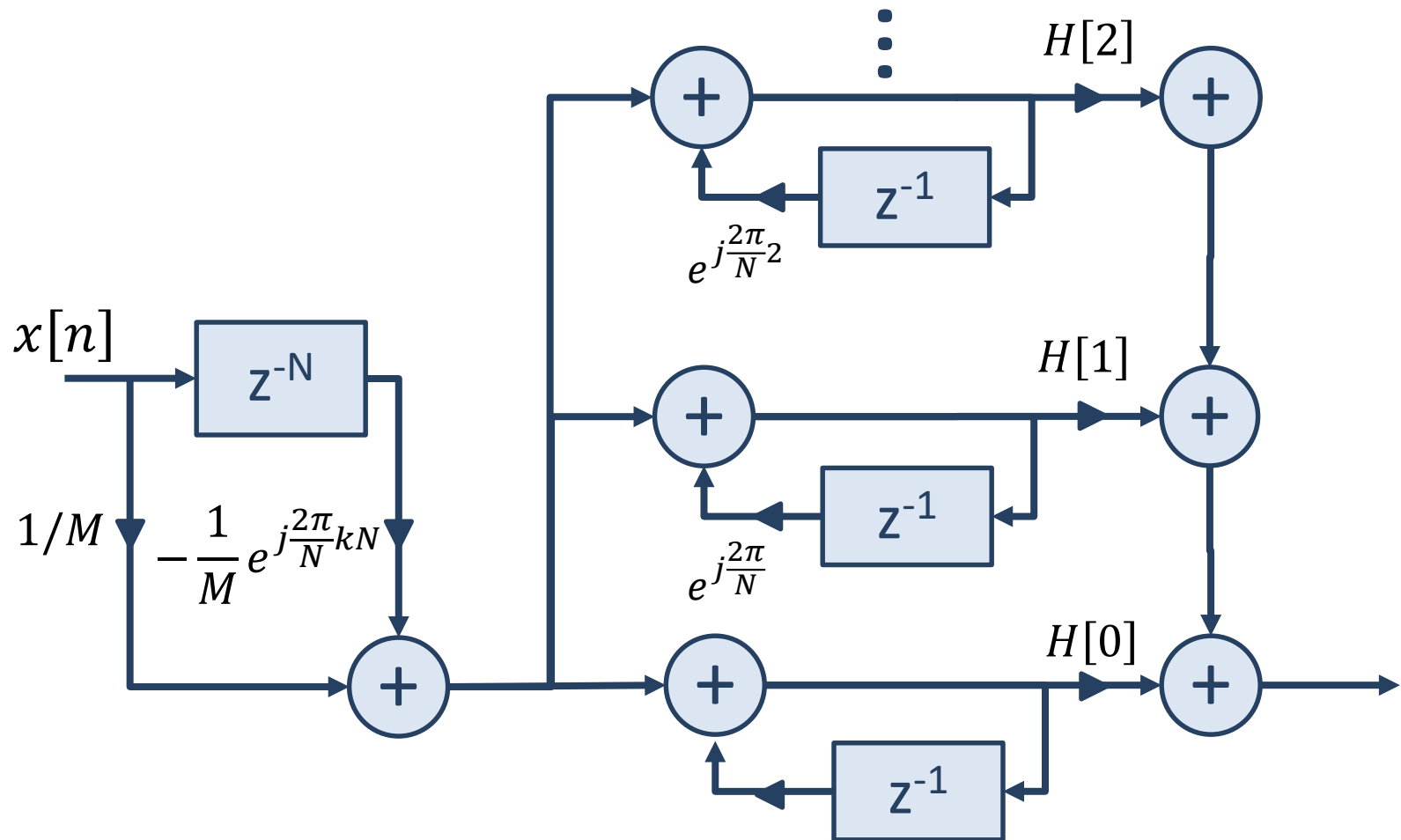

# Implementing FIR Filters
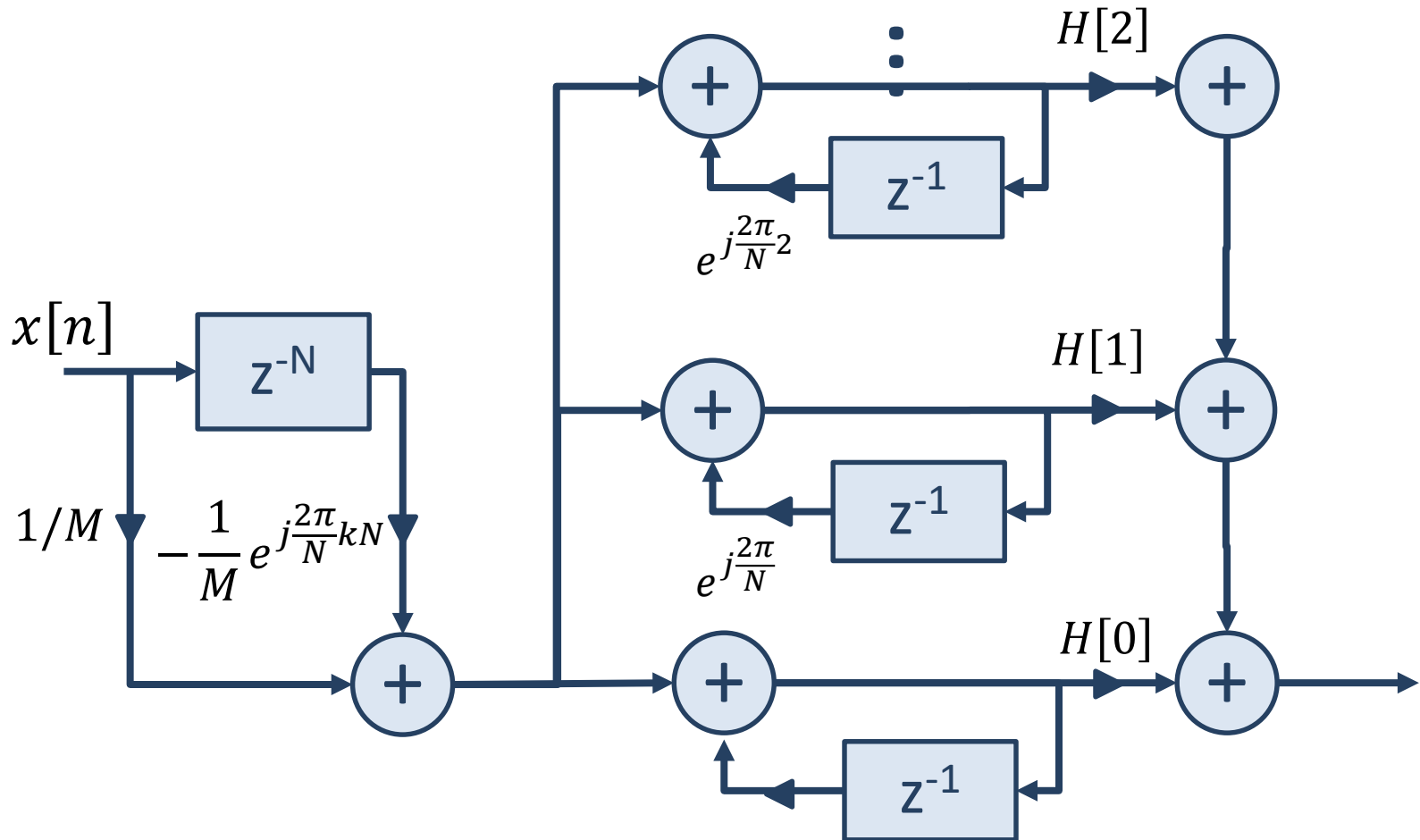
## ■ Frequency Sampling Form

- What are some benefits of using a cascade form implementation?



# Lecture 17: Lattice Structures

Foundations of Digital Signal Processing

## Outline

- Implementation of FIR Filters
- **Implementation of IIR Filters**
- Implementation of Lattice Filters



# Implementing IIR Filters

## ■ Two ways to look at IIR filters with only recursive components

### ■ Convolution perspective

$$y[n] + \sum_{m=1}^{M-1} g[m]y[n-m] = x[n]$$

### ■ Filtering perspective

$$Y(z) = \frac{X(z)}{1 + \sum_{m=1}^{M-1} g[m]z^{-m}}$$

# Implementing IIR Filters

## ■ Two ways to look at IIR filters with only recursive components

### ■ Convolution perspective

$$y[n] = x[n] - \sum_{m=1}^{M-1} g[m]y[n-m]$$

### ■ Filtering perspective

$$Y(z) = \frac{X(z)}{1 + \sum_{m=1}^{M-1} g[m]z^{-m}}$$

# Implementing IIR Filters


## ■ IIR Direct Form

$$y[n] = x[n] - \sum_{m=1}^{M-1} g[m]y[n-m]$$

# Implementing IIR Filters

## ■ IIR Direct Form ( $M = 1$ )


$$y[n] = x[n] - g[1]y[n - 1]$$

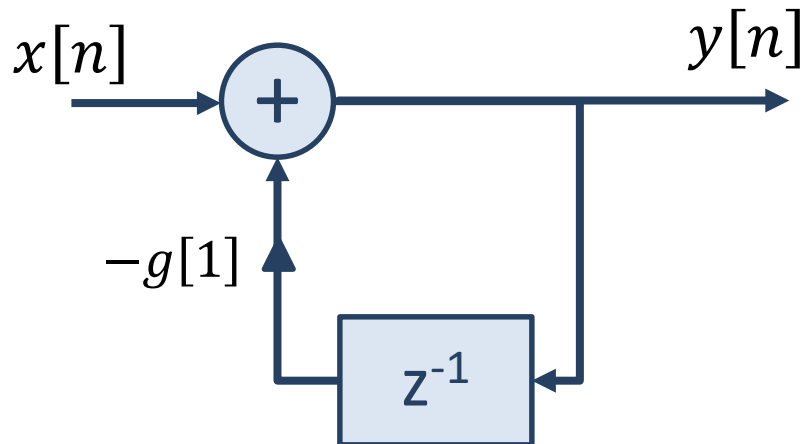

# Implementing IIR Filters
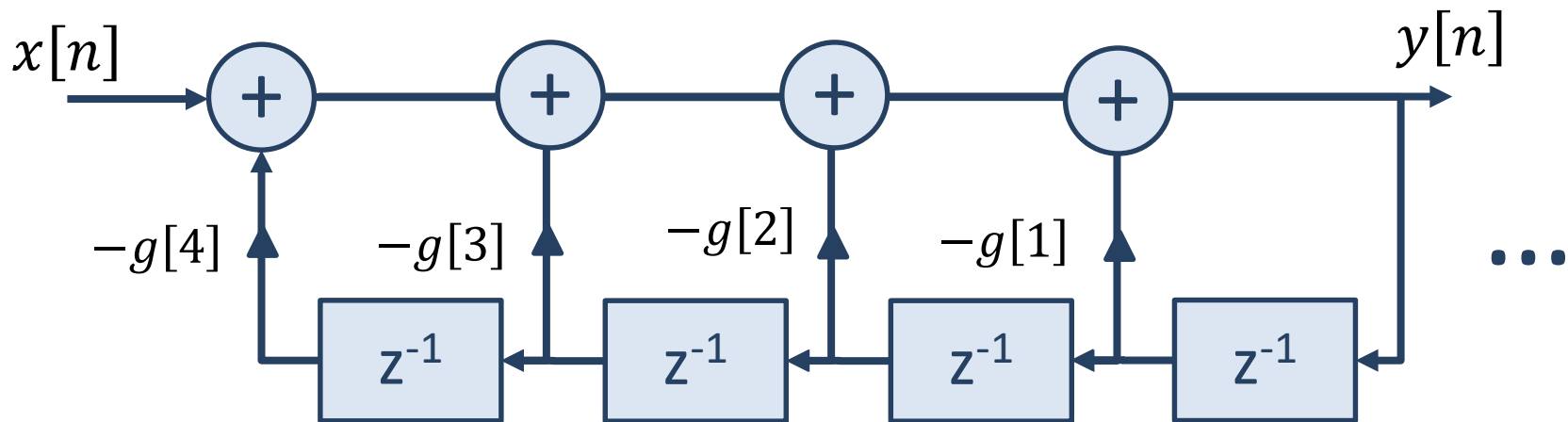
## ■ IIR Direct Form

$$y[n] = x[n] - \sum_{m=1}^{M-1} g[m]y[n-m]$$



# Implementing IIR Filters

## ■ Two ways to look at general IIR filters

### ■ Convolution perspective

$$y[n] + \sum_{m=1}^{M-1} g[m]y[n-m] = \sum_{k=1}^{M-1} h[k]x[n-k]$$

### ■ Filtering perspective

$$\frac{Y(z)}{X(z)} = \frac{\sum_{m=0}^{M-1} h[m]z^{-m}}{1 + \sum_{m=1}^{M-1} g[m]z^{-m}}$$

# Implementing IIR Filters

## ■ Two ways to look at general IIR filters

### ■ Convolution perspective

$$y[n] = \sum_{k=1}^{M-1} h[k]x[n-k] - \sum_{m=1}^{M-1} g[m]y[n-m]$$

### ■ Filtering perspective

$$\frac{Y(z)}{X(z)} = \frac{\sum_{m=0}^{M-1} h[m]z^{-m}}{1 + \sum_{m=0}^{M-1} g[m]z^{-m}}$$

# Implementing IIR Filters

## ■ Two ways to look at IIR filters with only recursive components

### ■ Convolution perspective

$$y[n] = x[n] - \sum_{m=1}^{M-1} g[m]y[n-m]$$


### ■ Filtering perspective

$$\frac{Y(z)}{X(z)} = \frac{\sum_{m=0}^{M-1} h[m]z^{-m}}{1 + \sum_{m=1}^{M-1} g[m]z^{-m}}$$




# Implementing IIR Filters

## ■ IIR Direct Form

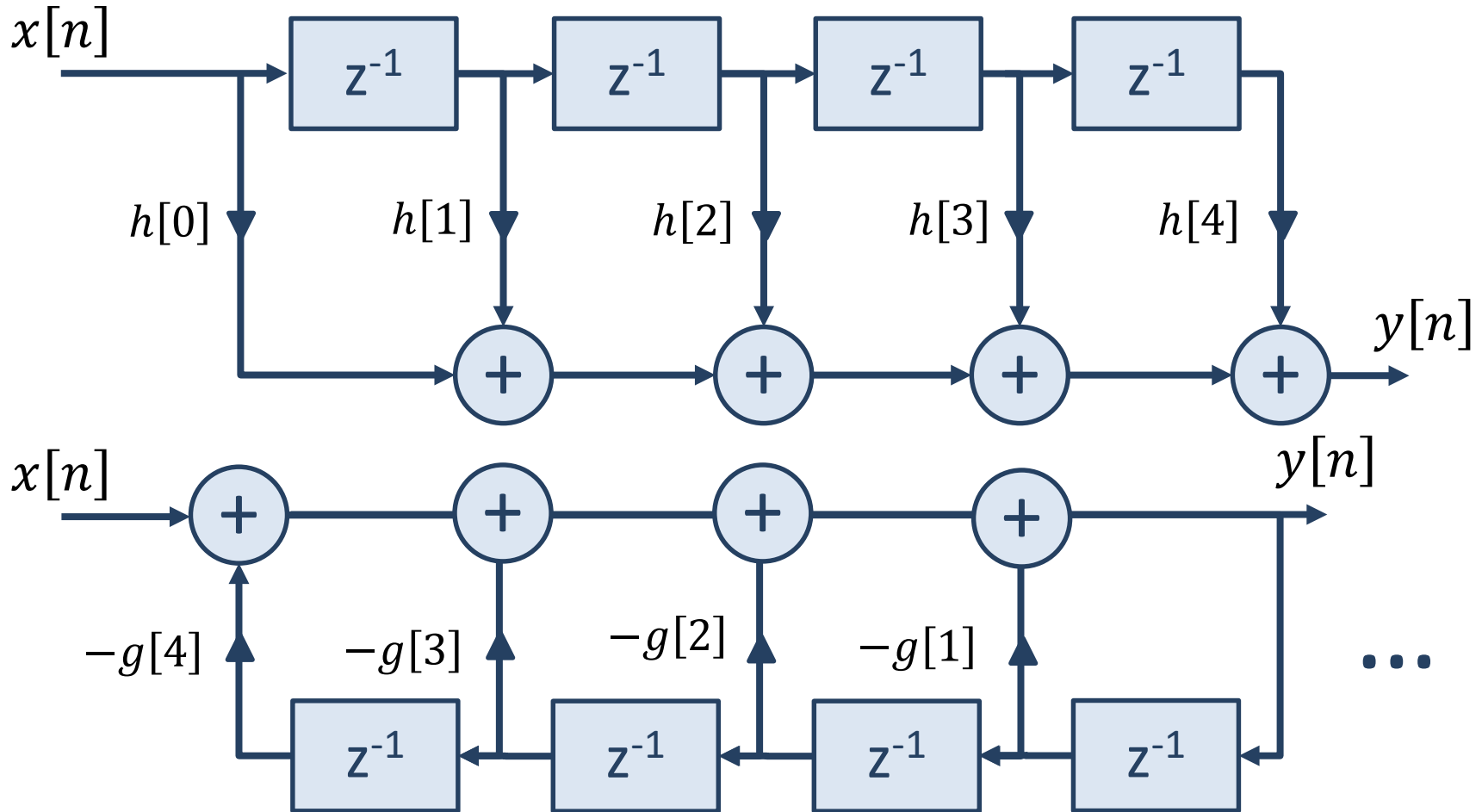


# Implementing IIR Filters

## ■ IIR Direct Form

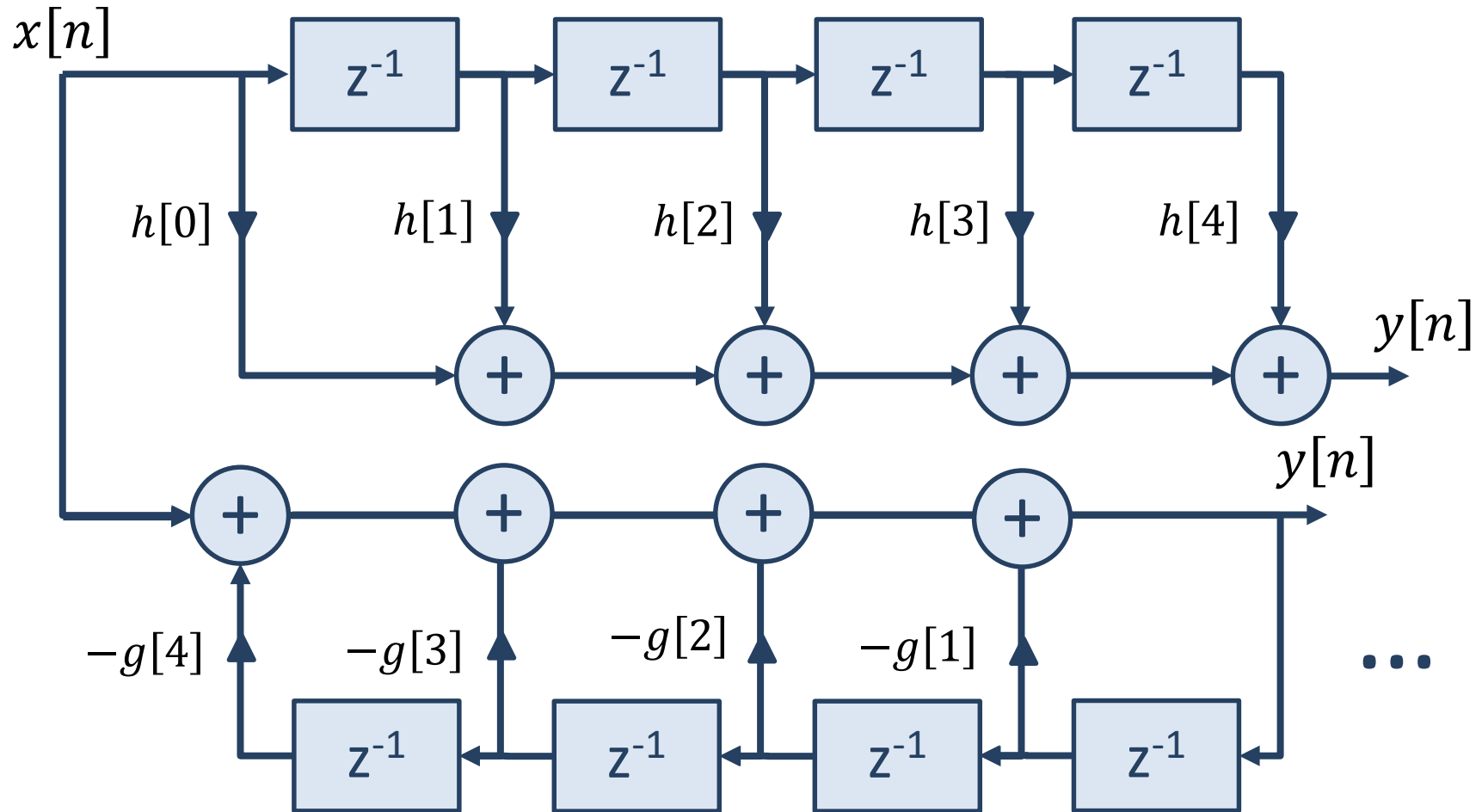


# Implementing IIR Filters

## ■ IIR Direct Form

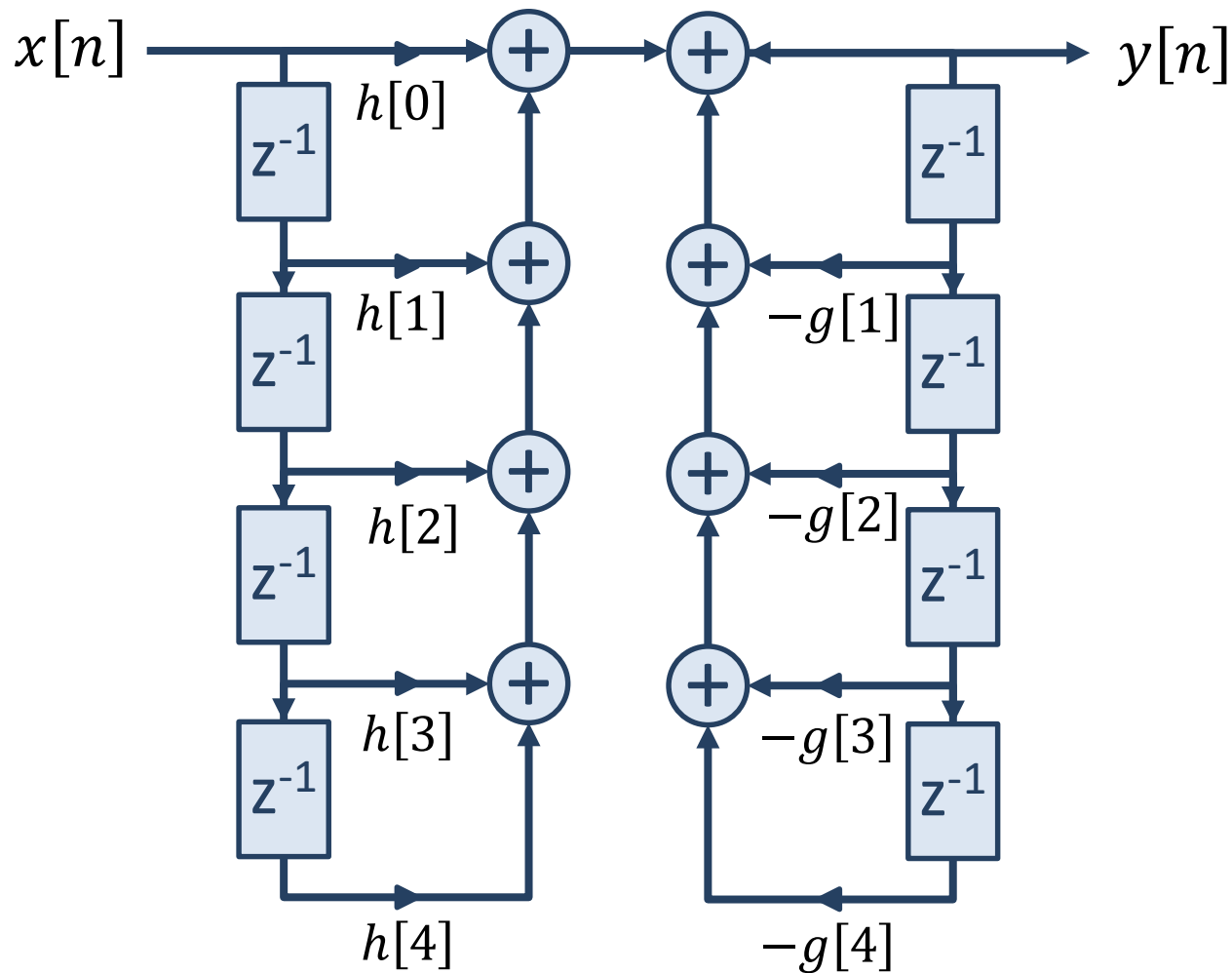


# Implementing IIR Filters

## ■ IIR Direct Form I

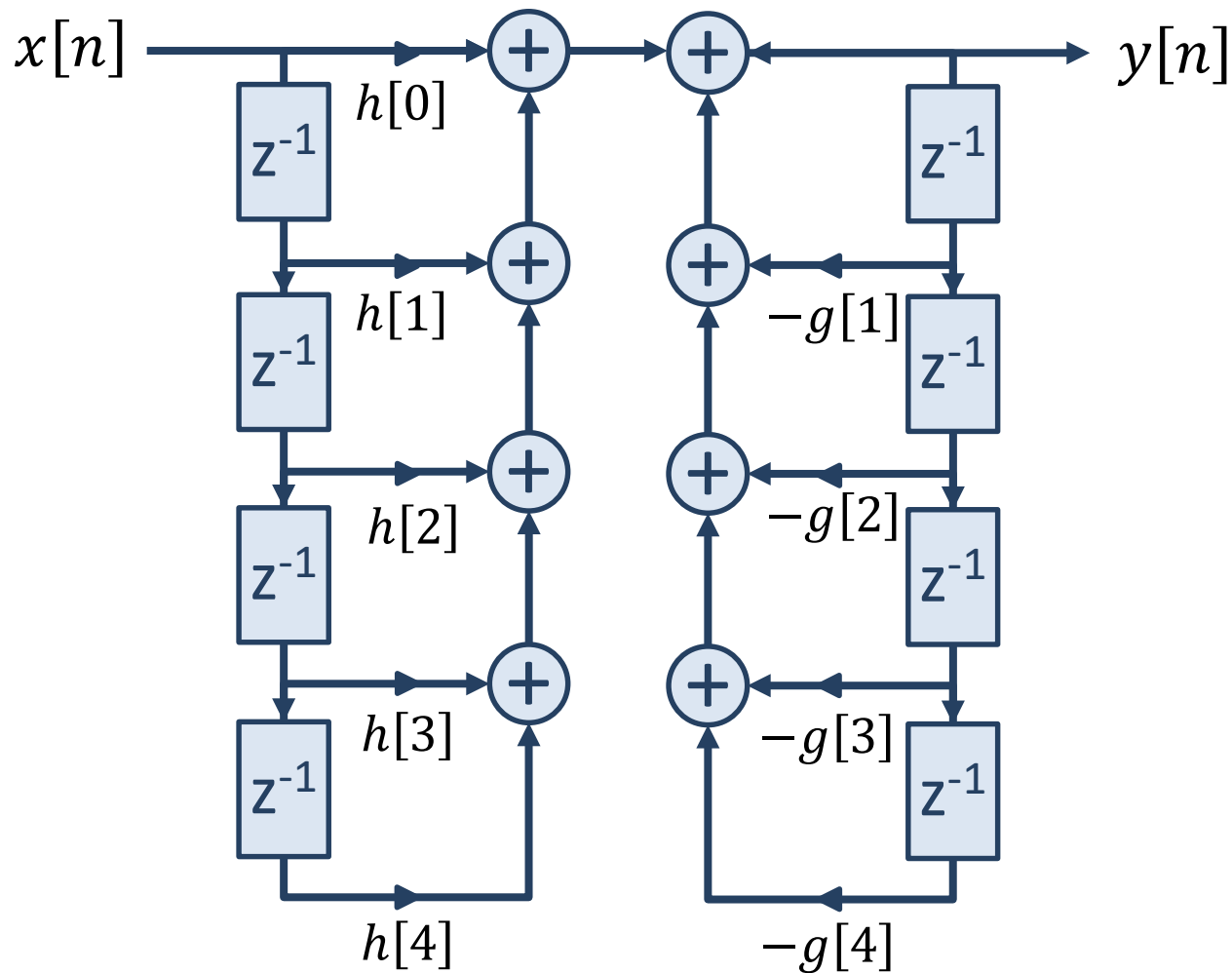


# Implementing IIR Filters

## ■ IIR Direct Form II (transition)

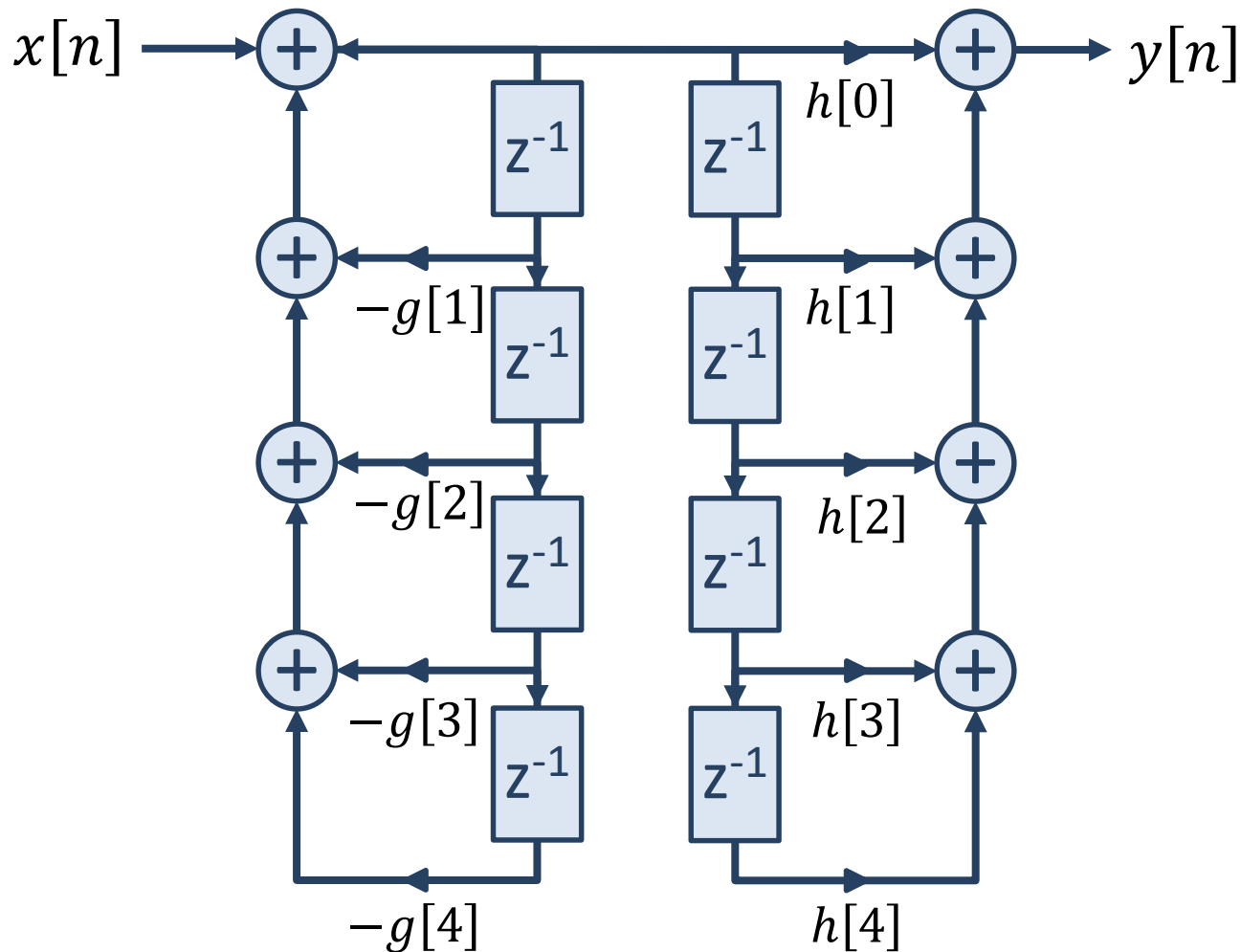


# Implementing IIR Filters

## ■ IIR Direct Form II

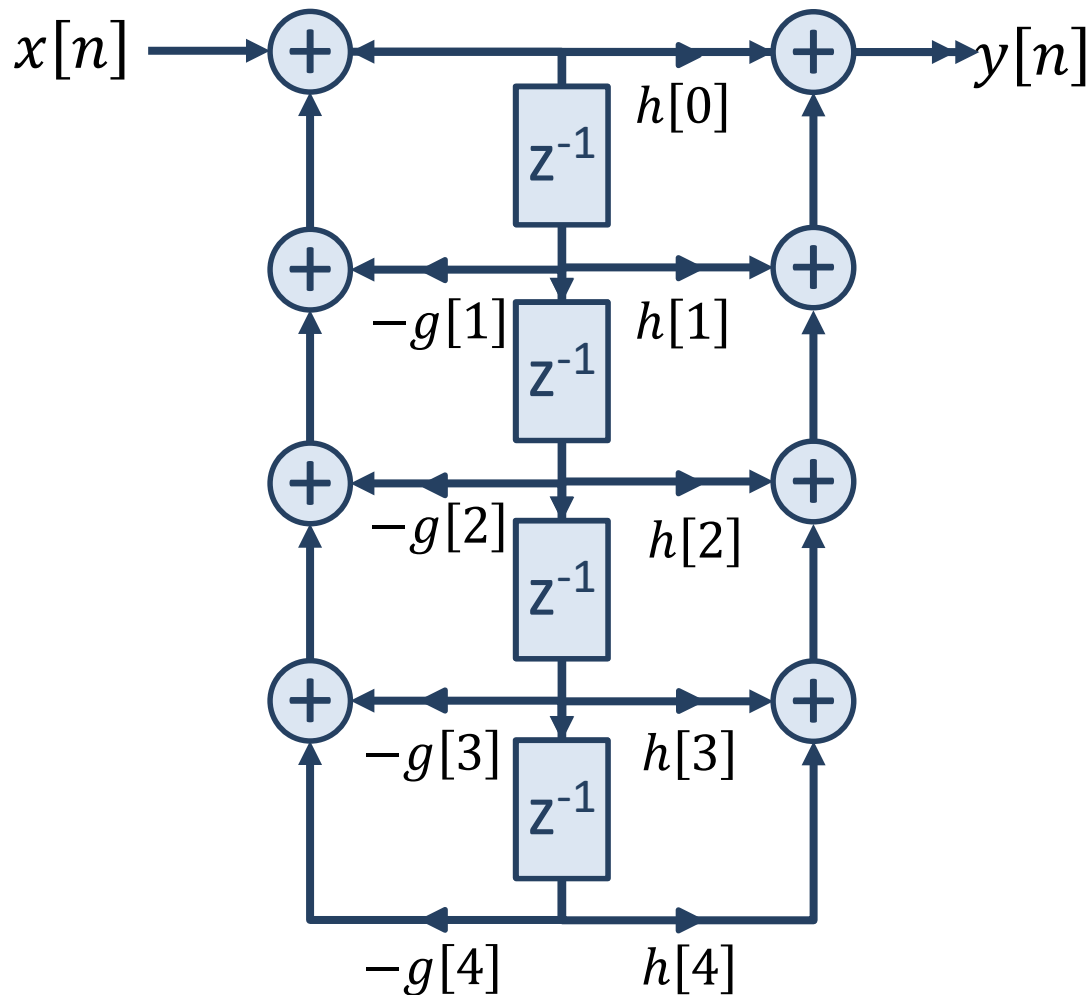


# Implementing IIR Filters

## ■ IIR Direct Form I

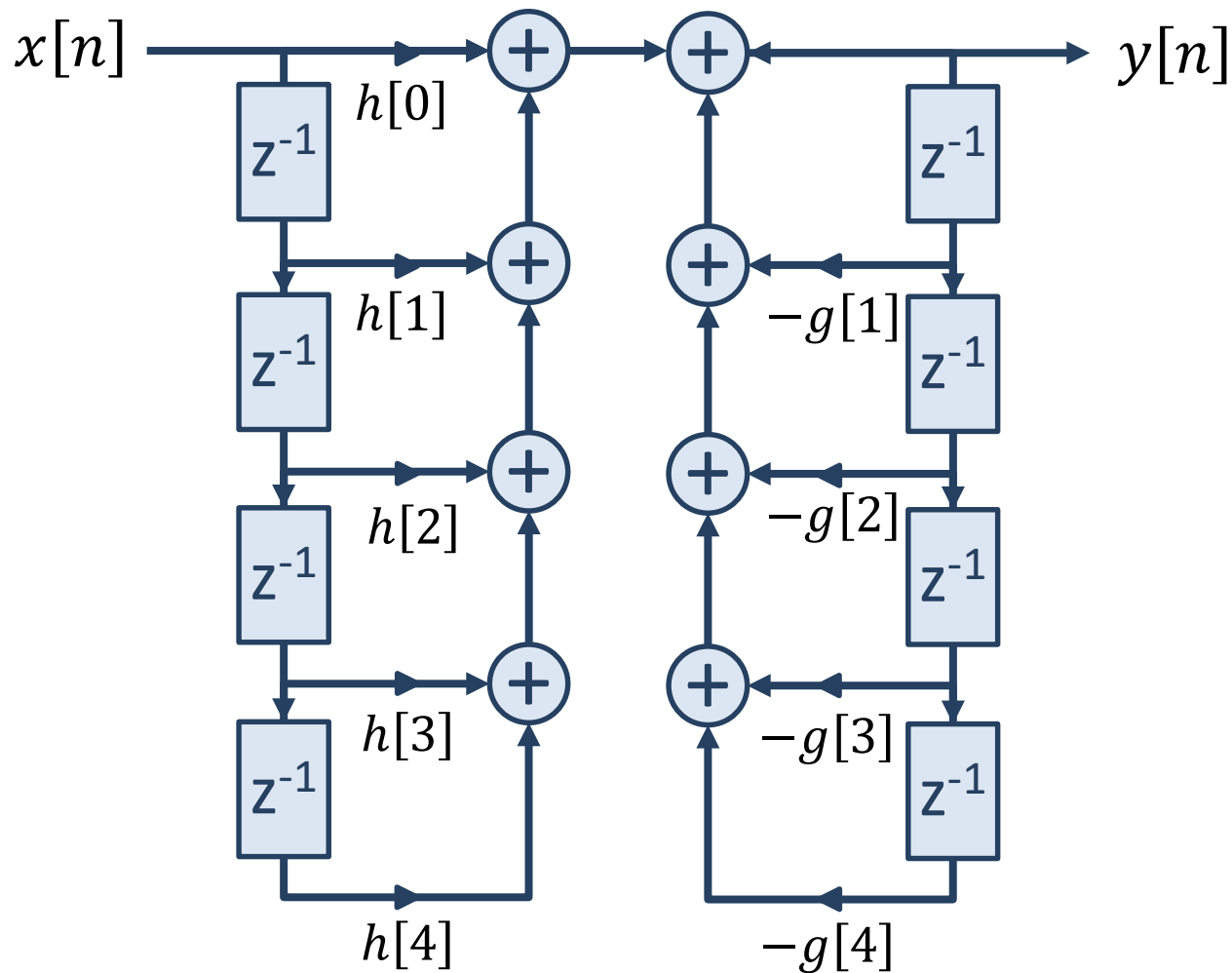

# Implementing IIR Filters

## ■ Transposed IIR Direct Form II


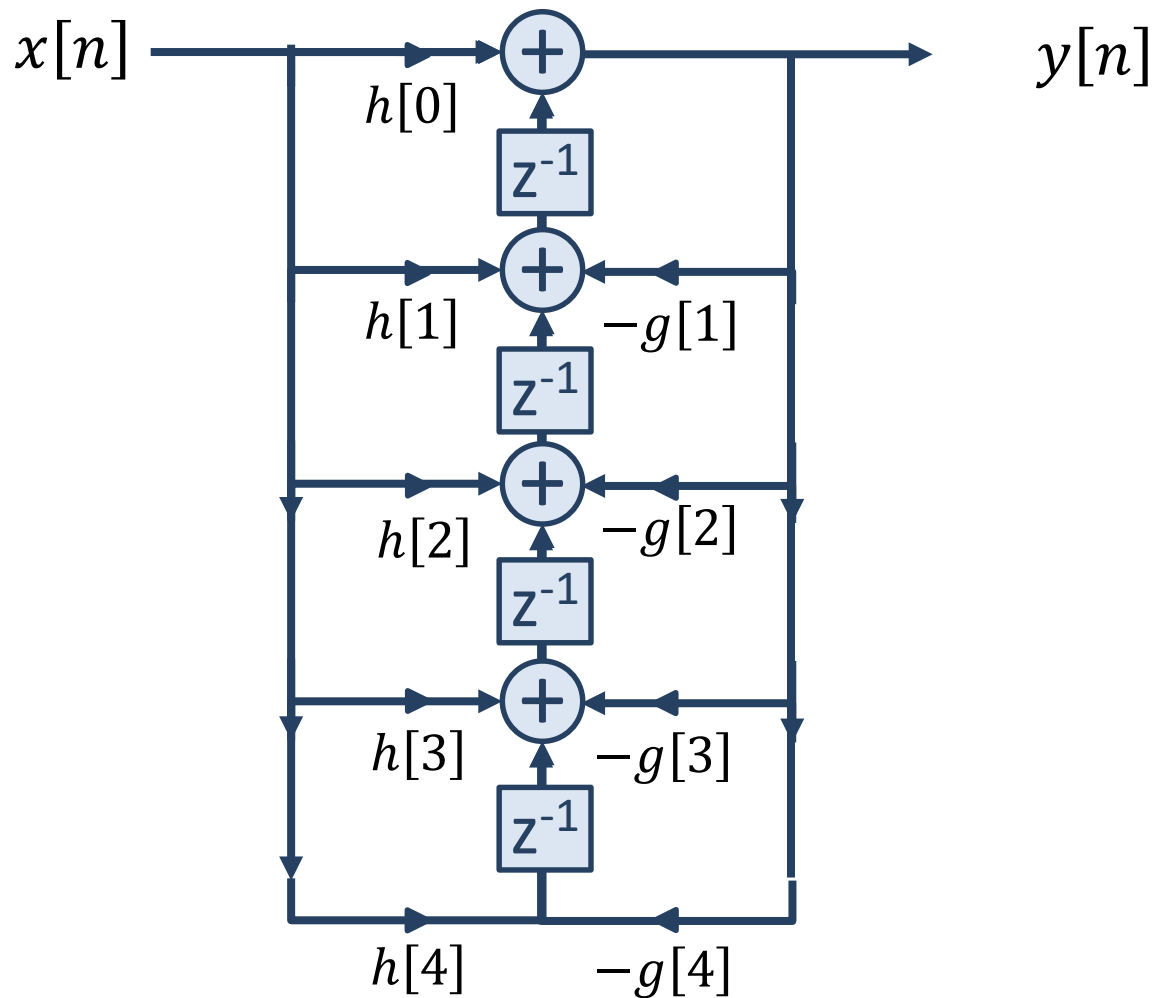




# Implementing FIR Filters
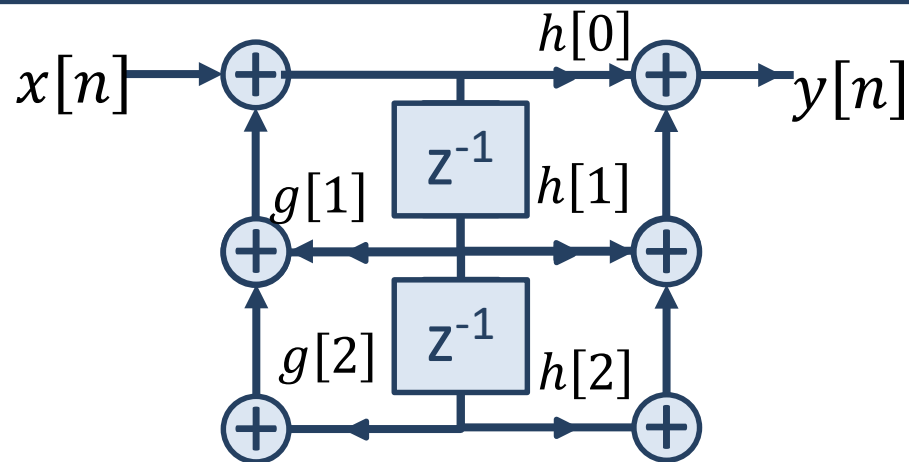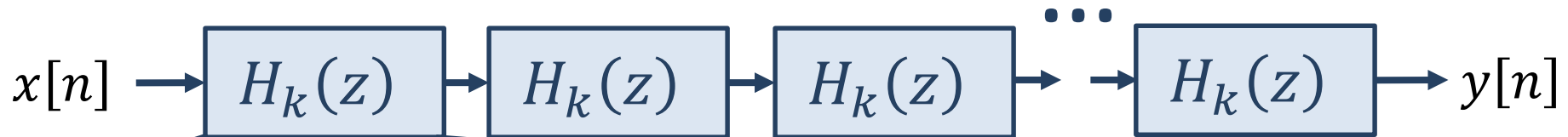
## ■ IIR Cascade Form


$$Y(z) = X(z) \sum_{m=0}^{M-1} h[m]z^{-m} = X(z) \prod_{k=1}^K H_k(z)$$



# Implementing FIR Filters
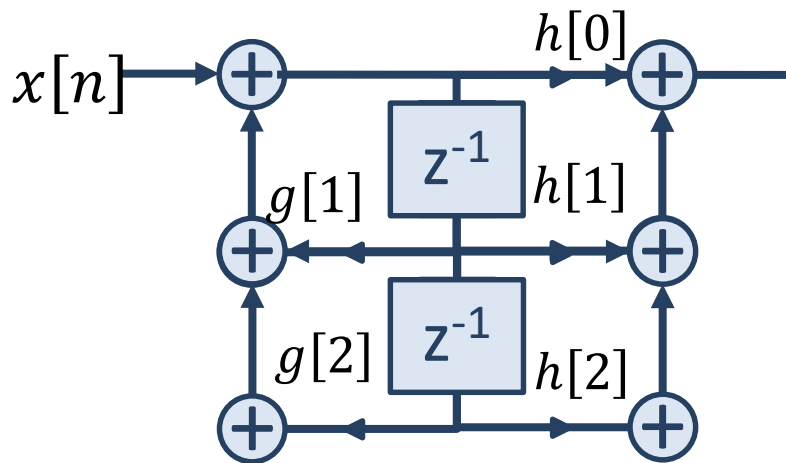
## ■ IIR Cascade Form


$$Y(z) = X(z) \sum_{m=0}^{M-1} h[m]z^{-m} = X(z) \prod_{k=1}^K H_k(z)$$



# Implementing FIR Filters
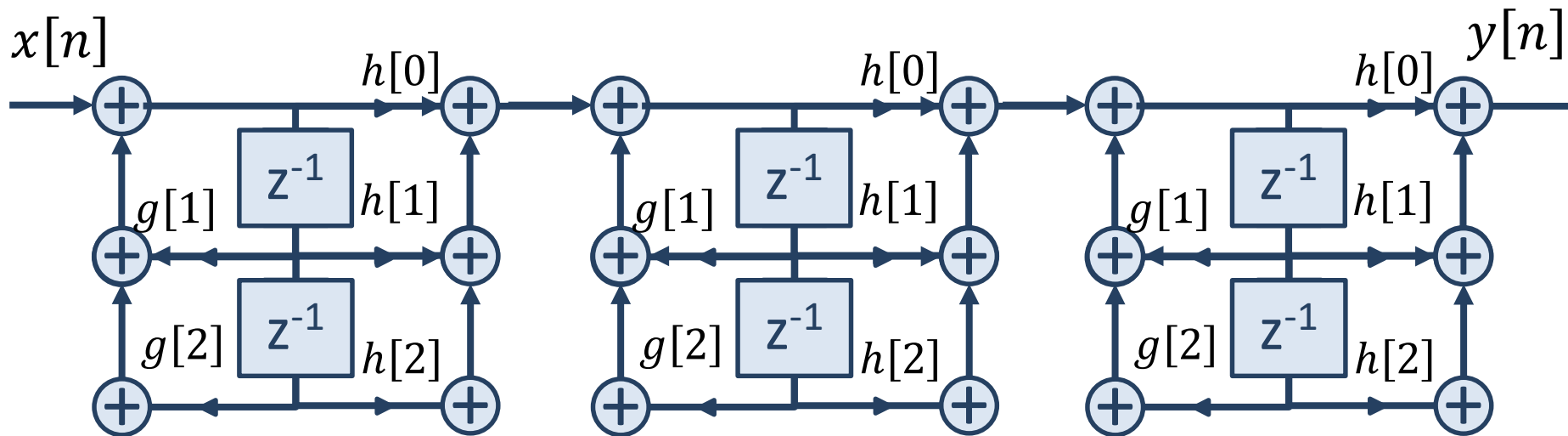
## ■ IIR Cascade Form

$$Y(z) = X(z) \sum_{m=0}^{M-1} h[m]z^{-m} = X(z) \prod_{k=1}^K H_k(z)$$




# Implementing IIR Filters

## ■ Parallel Form

$$H(z) = C + \sum_{m=0}^{M-1} \frac{a[m]}{1 - p_m z^{-1}}$$

From partial fraction decomposition

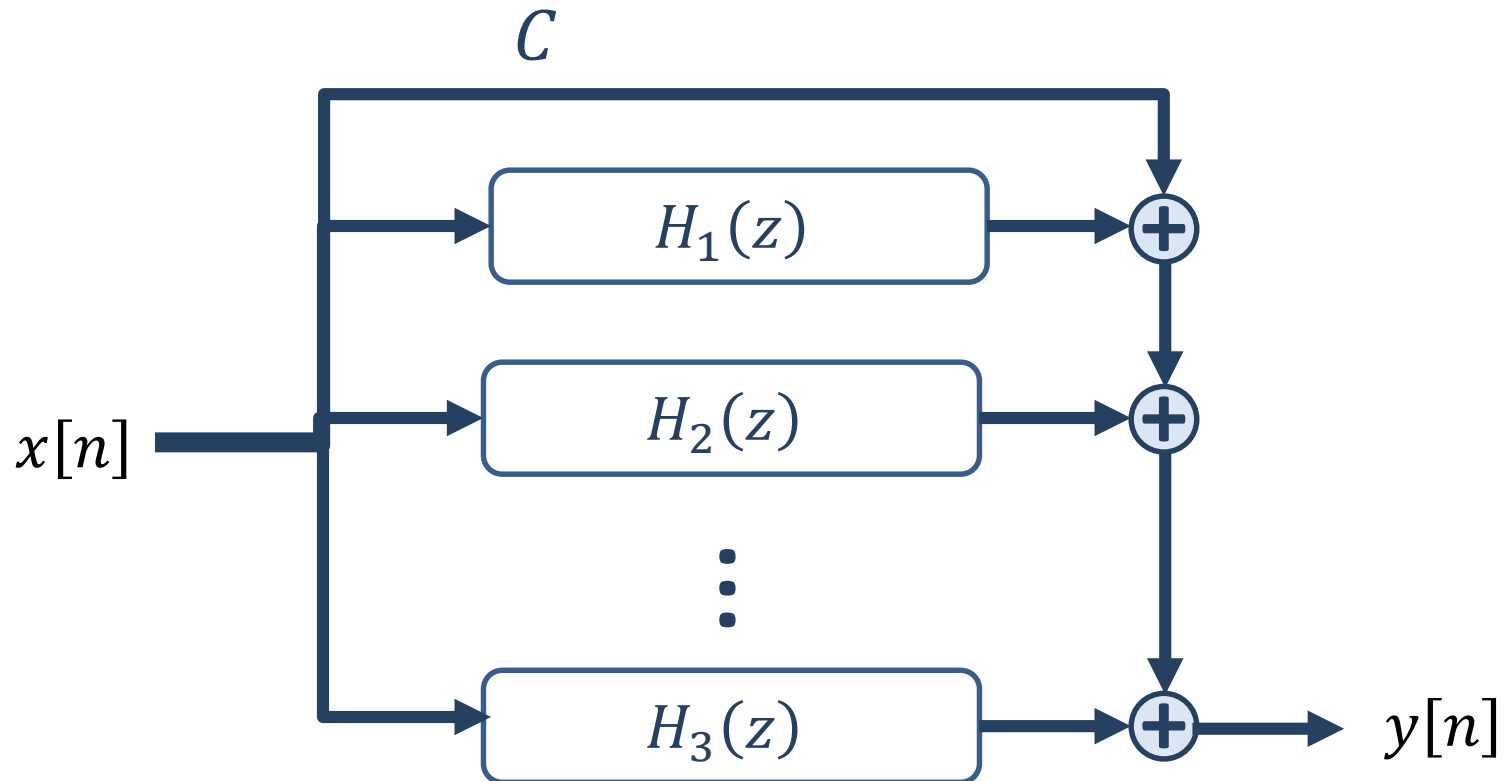

# Lecture 17: Lattice Structures

## Foundations of Digital Signal Processing

### Outline

- Implementation of FIR Filters
- Implementation of IIR Filters
- **Implementation of Lattice Filters**


# Implementing Lattice Filters

## ■ Lattice Stage

- **Question:** What is the transfer function?

$$y[n] = Kv[n] + u[n - 1]$$

$$v[n] = x[n] - Ku[n - 1]$$

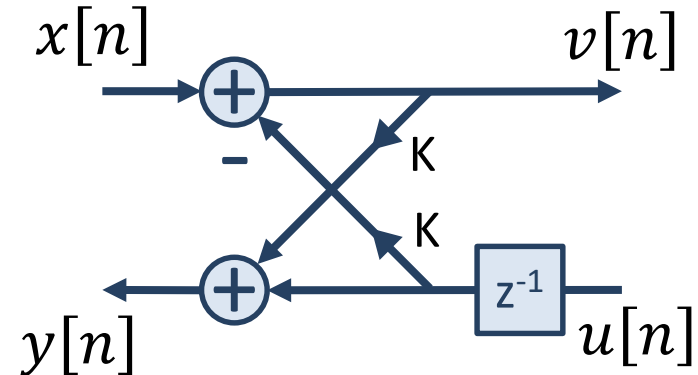


# Implementing Lattice Filters

## ■ Lattice Stage

- **Question:** What is the transfer function?

$$Y(z) = KV(z) + U(z)z^{-1}$$

$$V(z) = X(z) - KU(z)z^{-1}$$

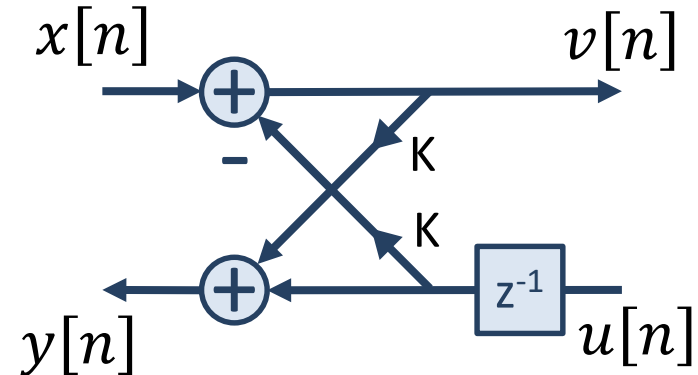

# Implementing Lattice Filters


## ■ Lattice Stage

- **Question:** What is the transfer function?

$$Y(z) = KV(z) + U(z)z^{-1}$$

$$V(z) = X(z) - KU(z)z^{-1}$$

$$\frac{Y(z)}{X(z)} = ?$$

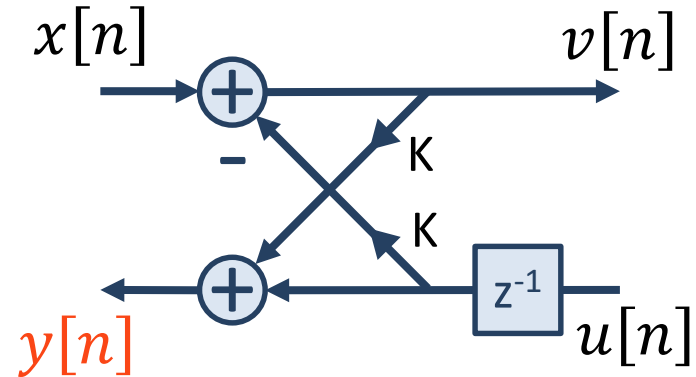



# Implementing Lattice Filters


## ■ Lattice Stage

- **Question:** What is the transfer function?

$$Y(z) = KV(z) + U(z)z^{-1}$$

$$X(z) = V(z) + KU(z)z^{-1}$$

$$\frac{Y(z)}{X(z)} = ?$$

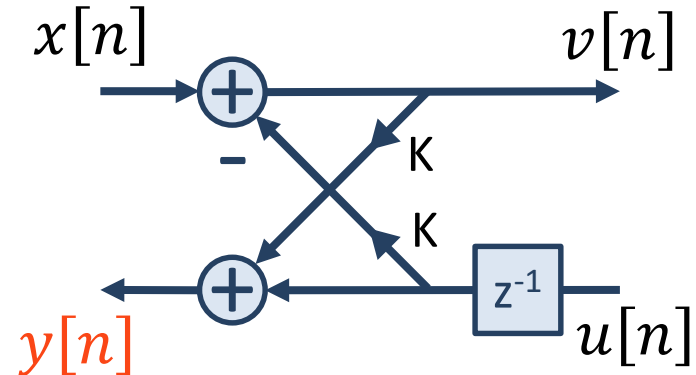

# Implementing Lattice Filters


## ■ Lattice Stage

- **Question:** What is the transfer function?

$$Y(z) = KV(z) + U(z)z^{-1}$$

$$X(z) = V(z) + KU(z)z^{-1}$$
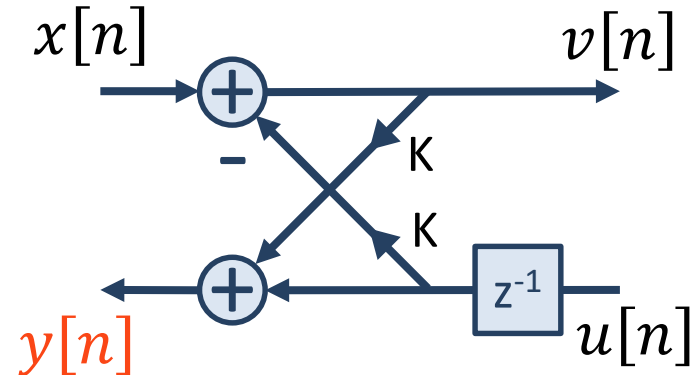
$$\frac{Y(z)}{X(z)} = \frac{KV(z) + U(z)z^{-1}}{V(z) + KU(z)z^{-1}}$$



# Implementing Lattice Filters


## ■ Lattice Stage

- **Question:** What is the transfer function?

$$Y(z) = KV(z) + V(z)z^{-1}$$

$$X(z) = V(z) + KV(z)z^{-1}$$
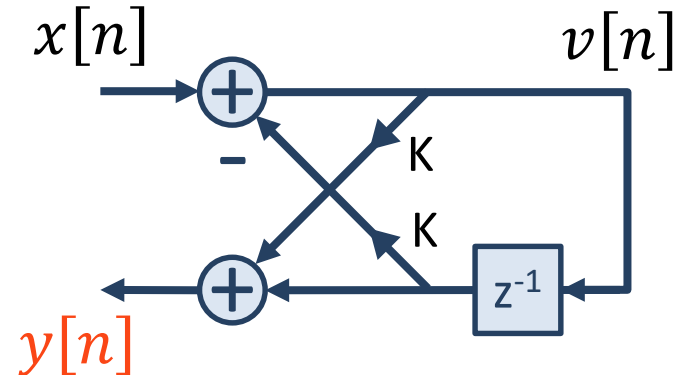
$$\frac{Y(z)}{X(z)} = \frac{KV(z) + V(z)z^{-1}}{V(z) + KV(z)z^{-1}}$$




# Implementing Lattice Filters

## ■ Lattice Stage

- **Question:** What is the transfer function?

$$Y(z) = [K + z^{-1}]V(z)$$

$$X(z) = [1 + Kz^{-1}]V(z)$$

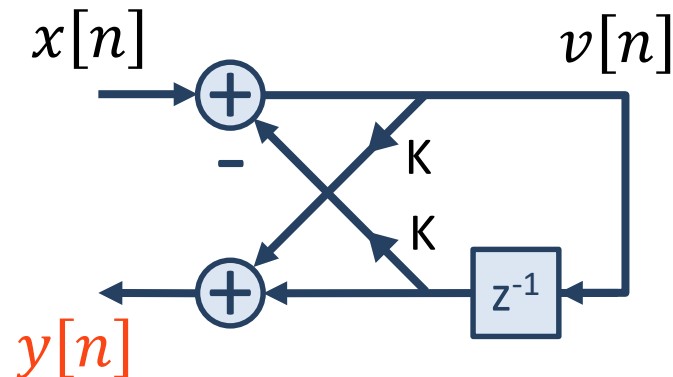

$$\frac{Y(z)}{X(z)} = \frac{KV(z) + V(z)z^{-1}}{V(z) + KV(z)z^{-1}}$$


# Implementing Lattice Filters

## ■ Lattice Stage

- **Question:** What is the transfer function?

$$Y(z) = [K + z^{-1}]V(z)$$

$$X(z) = [1 + Kz^{-1}]V(z)$$

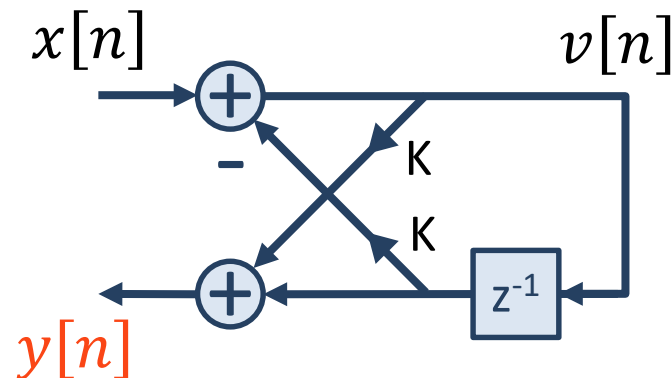

$$\frac{Y(z)}{X(z)} = \frac{KV(z) + V(z)z^{-1}}{V(z) + KV(z)z^{-1}} = \frac{K + z^{-1}}{1 + Kz^{-1}}$$

**Question:** What kind of filter is this?


# Implementing Lattice Filters

## ■ Lattice Stage

- **Question:** What is the transfer function?

$$Y(z) = [K + z^{-1}]V(z)$$

$$X(z) = [1 + Kz^{-1}]V(z)$$

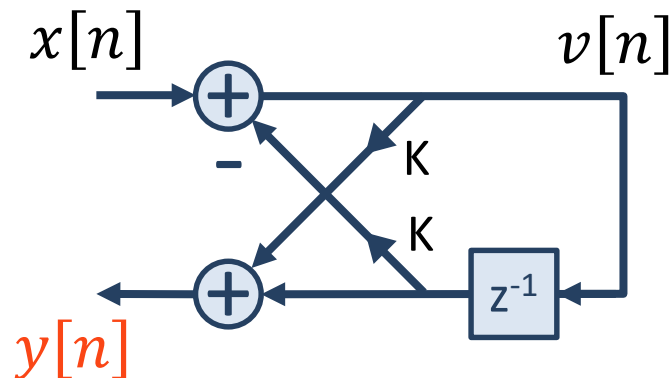

$$\frac{Y(z)}{X(z)} = \frac{KV(z) + V(z)z^{-1}}{V(z) + KV(z)z^{-1}} = \frac{K + z^{-1}}{1 + Kz^{-1}}$$

**Question:** What kind of filter is this? **All-Pass Filter**

# Implementing Lattice Filters


## ■ Lattice Stage

- **Question:** What is the transfer function?

$$Y(z) = [K + z^{-1}]V(z)$$

$$X(z) = [1 + Kz^{-1}]V(z)$$

$$\frac{V(z)}{X(z)} = ?$$

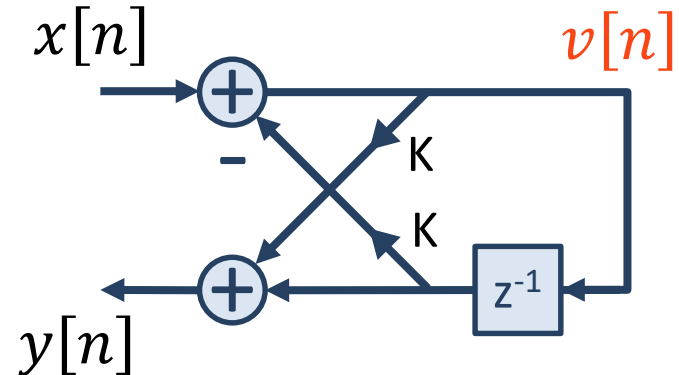


# Implementing Lattice Filters

## ■ Lattice Stage

- **Question:** What is the transfer function?

$$Y(z) = [K + z^{-1}]V(z)$$

$$X(z) = [1 + Kz^{-1}]V(z)$$

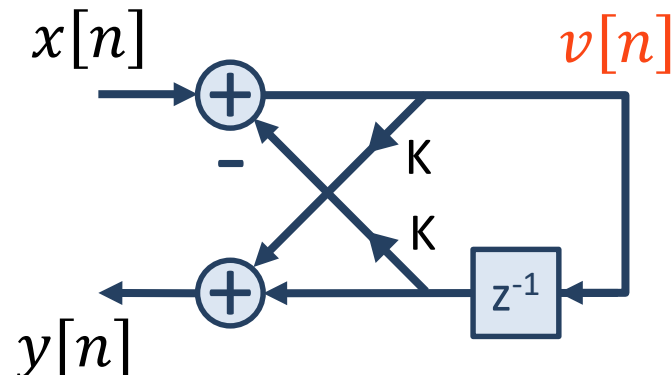

$$\frac{V(z)}{X(z)} = \frac{1}{1 + Kz^{-1}}$$

**Question:** What kind of filter is this?




# Implementing Lattice Filters

## ■ Lattice Stage

- **Question:** What is the transfer function?

$$Y(z) = [K + z^{-1}]V(z)$$

$$X(z) = [1 + Kz^{-1}]V(z)$$

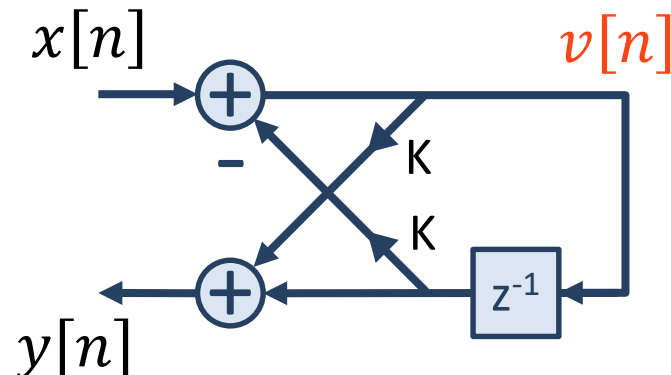

$$\frac{V(z)}{X(z)} = \frac{1}{1 + Kz^{-1}}$$

**Question:** What kind of filter is this? **IIR Filter**

# Implementing Lattice Filters


## ■ Lattice Stage

- **Question:** What is the transfer function?

$$Y(z) = [K + z^{-1}]V(z)$$

$$X(z) = [1 + Kz^{-1}]V(z)$$

$$\frac{Y(z)}{V(z)} = ?$$

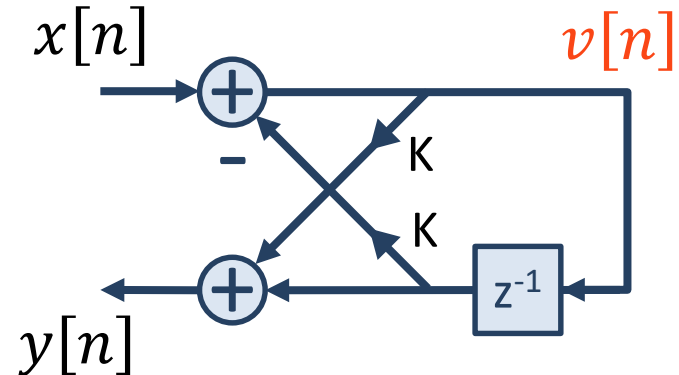

# Implementing Lattice Filters


## ■ Lattice Stage

- **Question:** What is the transfer function?

$$Y(z) = [K + z^{-1}]V(z)$$

$$X(z) = [1 + Kz^{-1}]V(z)$$

$$\frac{Y(z)}{V(z)} = 1 + Kz^{-1}$$

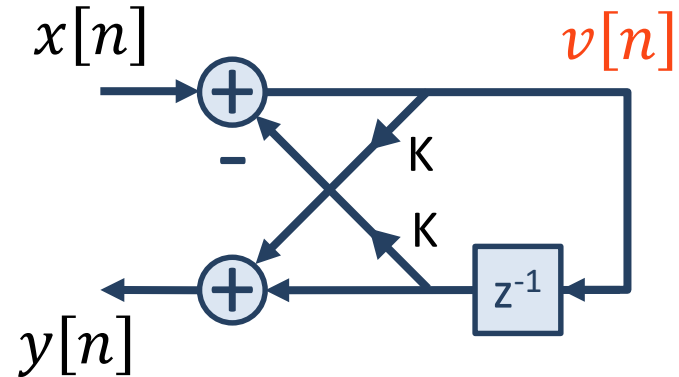

**Question:** What kind of filter is this?

# Implementing Lattice Filters


## ■ Lattice Stage

- **Question:** What is the transfer function?

$$Y(z) = [K + z^{-1}]V(z)$$

$$X(z) = [1 + Kz^{-1}]V(z)$$

$$\frac{Y(z)}{V(z)} = 1 + Kz^{-1}$$

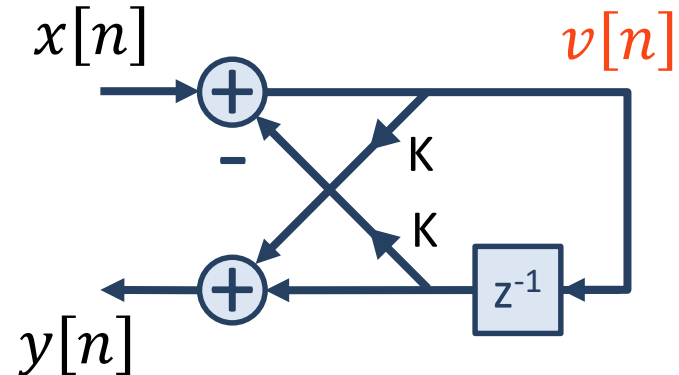


**Question:** What kind of filter is this? **FIR Filter**

# Implementing Lattice Filters

## ■ Lattice Stage

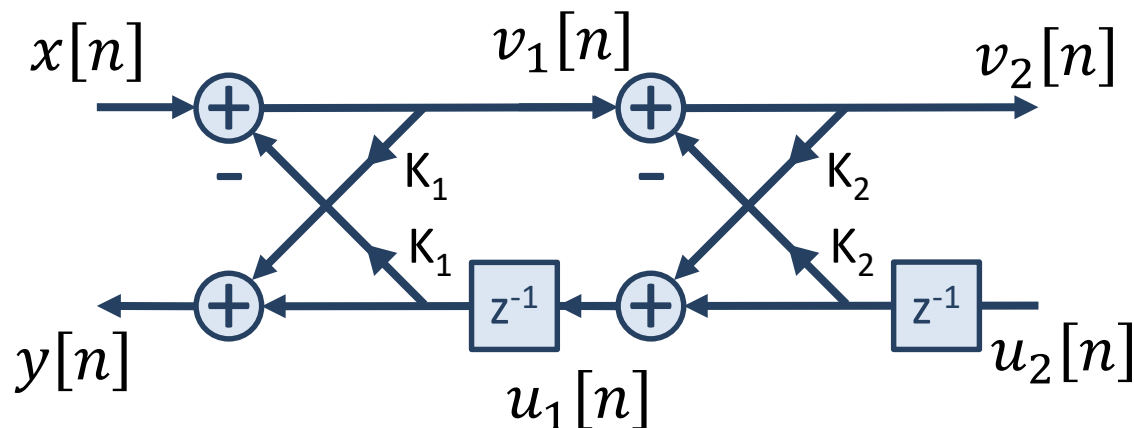- **Question:** What is the transfer function?



$$Y(z) = K_1 V_1(z) + U_1(z)z^{-1}$$

$$X(z) = V_1(z) + K_1 U_1(z)z^{-1}$$


$$U_1(z) = K_2 V_2(z) + U_2(z)z^{-1}$$

$$V_1(z) = V_2(z) + K_2 U_2(z)z^{-1}$$

# Implementing Lattice Filters

## ■ Lattice Stage

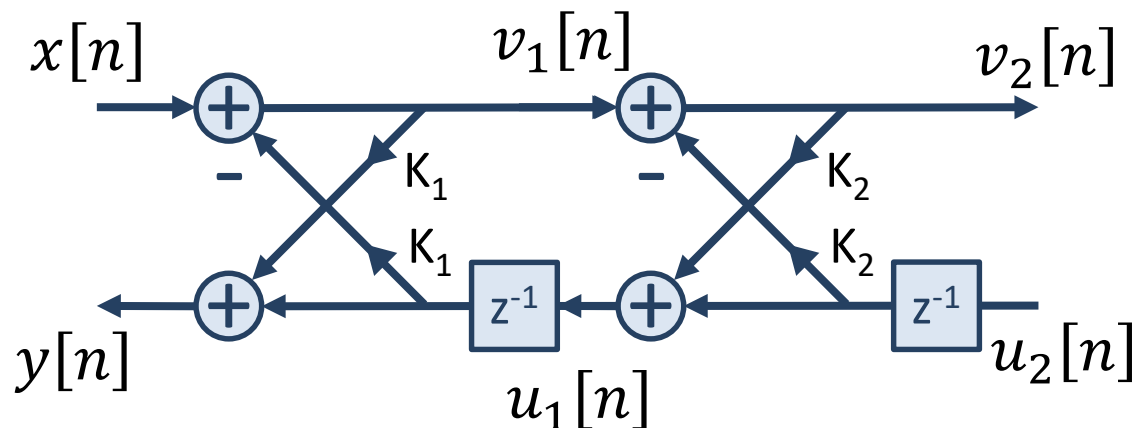- **Question:** What is the transfer function?




$$Y(z) = K_1[V_2(z) + K_2U_2(z)z^{-1}] + [K_2V_2(z) + U_2(z)z^{-1}]z^{-1}$$

$$X(z) = [V_2(z) + K_2U_2(z)z^{-1}] + K_1[K_2V_2(z) + U_2(z)z^{-1}]z^{-1}$$

# Implementing Lattice Filters

## ■ Lattice Stage

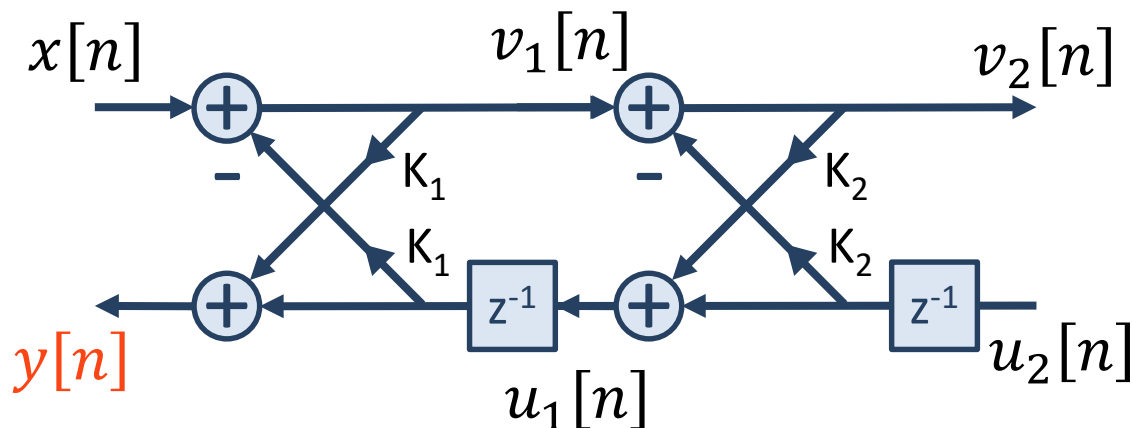- **Question:** What is the transfer function?



$$Y(z) = K_1[V_2(z) + K_2U_2(z)z^{-1}] + [K_2V_2(z) + U_2(z)z^{-1}]z^{-1}$$


$$X(z) = [V_2(z) + K_2U_2(z)z^{-1}] + K_1[K_2V_2(z) + U_2(z)z^{-1}]z^{-1}$$

$$\frac{Y(z)}{X(z)} = ?$$

# Implementing Lattice Filters

## ■ Lattice Stage

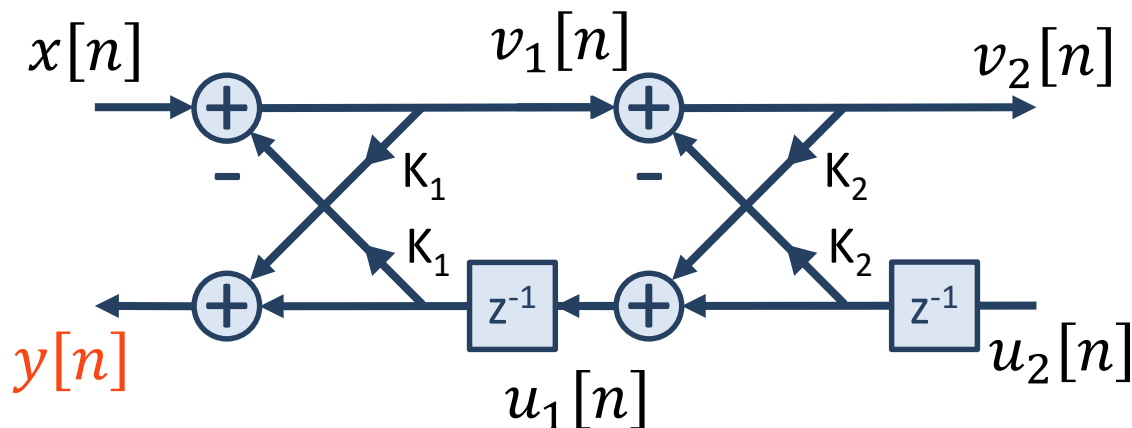- **Question:** What is the transfer function?



$$Y(z) = K_1 V_2(z) + K_1 K_2 U_2(z) z^{-1} + K_2 V_2(z) z^{-1} + U_2(z) z^{-2}$$

$$X(z) = V_2(z) + K_2 U_2(z) z^{-1} + K_1 K_2 V_2(z) z^{-1} + K_1 U_2(z) z^{-2}$$


$$\frac{Y(z)}{X(z)} = ?$$



# Implementing Lattice Filters

## ■ Lattice Stage

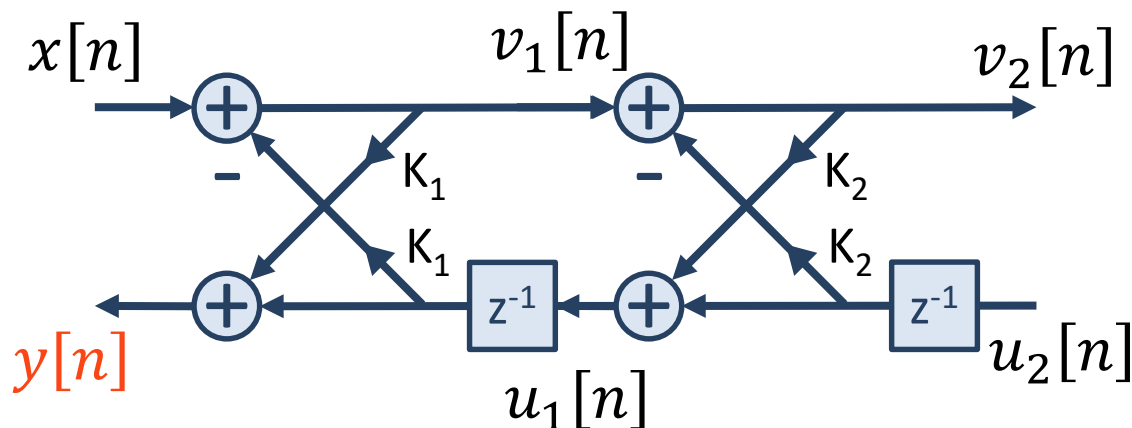- **Question:** What is the transfer function?



$$Y(z) = K_1 V_2(z) + [K_1 K_2 V_2(z) + K_2 V_2(z)] z^{-1} + V_2(z) z^{-2}$$


$$X(z) = V_2(z) + [K_2 U_2(z) + K_1 K_2 V_2(z)] z^{-1} + K_1 U_2(z) z^{-2}$$

$$\frac{Y(z)}{X(z)} = ?$$

# Implementing Lattice Filters

## ■ Lattice Stage

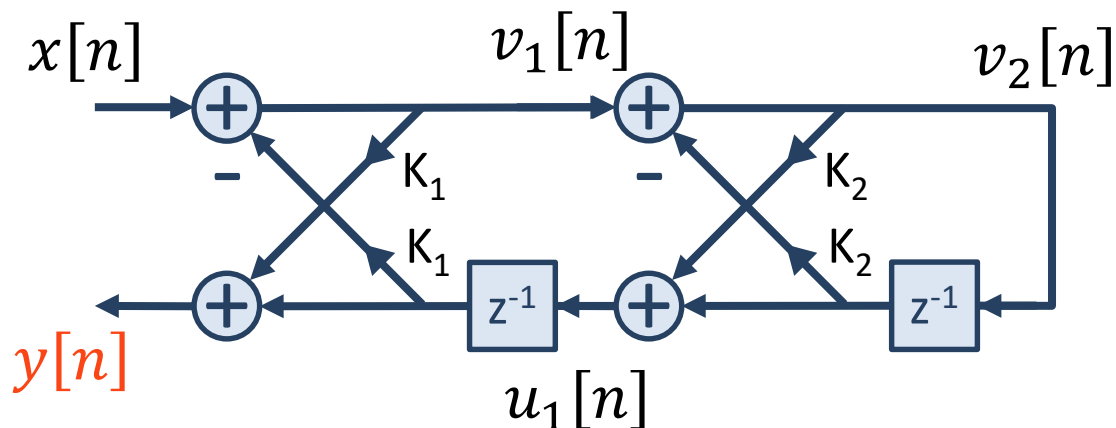- **Question:** What is the transfer function?



$$Y(z) = V_2(z)[K_1 + (K_1K_2 + K_2)z^{-1} + z^{-2}]$$


$$X(z) = V_2(z)[1 + (K_2 + K_1K_2)z^{-1} + K_1z^{-2}]$$

$$\frac{Y(z)}{X(z)} = ?$$

# Implementing Lattice Filters

## ■ Lattice Stage

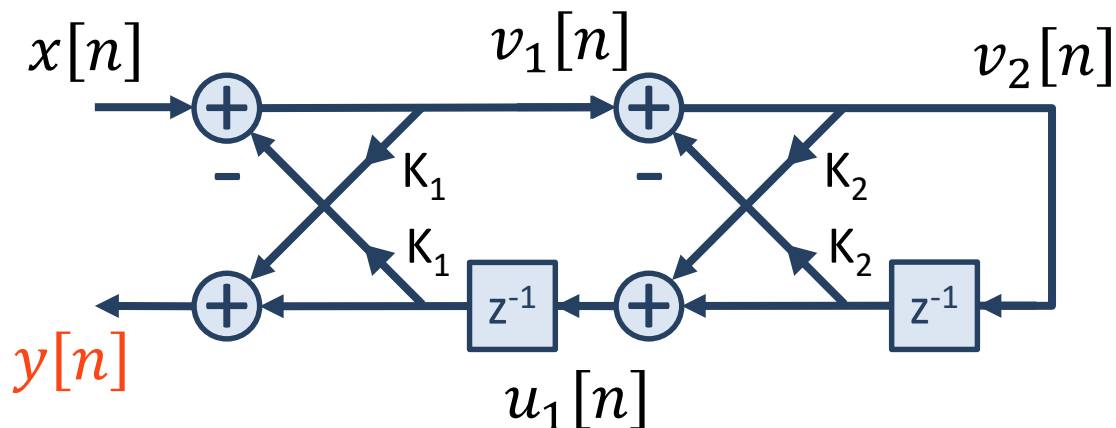- **Question:** What is the transfer function?



$$Y(z) = V_2(z)[K_1 + (K_1K_2 + K_2)z^{-1} + z^{-2}]$$


$$X(z) = V_2(z)[1 + (K_2 + K_1K_2)z^{-1} + K_1z^{-2}]$$

$$\frac{Y(z)}{X(z)} = \frac{K_1 + (K_2 + K_1K_2)z^{-1} + z^{-2}}{1 + (K_2 + K_1K_2)z^{-1} + K_1z^{-2}} = \frac{z^{-2}A(z^{-1})}{A(z)}$$

# Implementing Lattice Filters

## ■ Lattice Stage

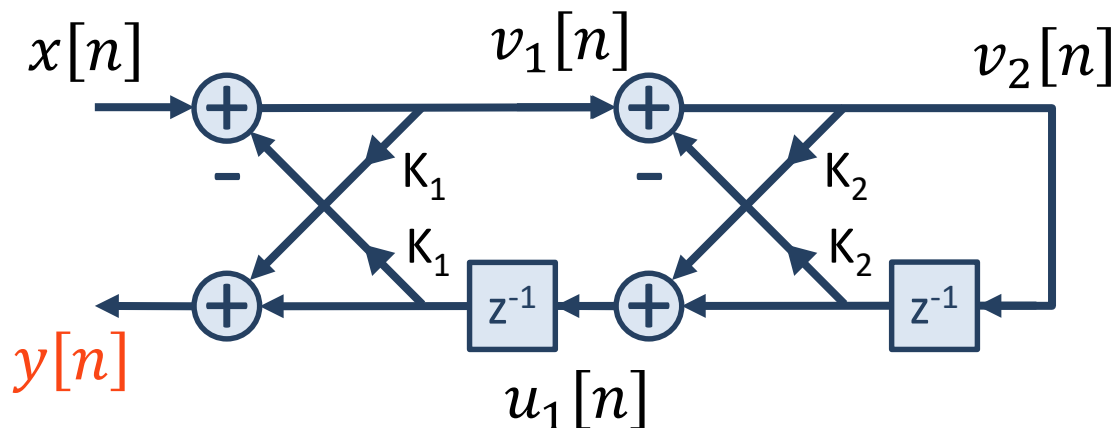- **Question:** What is the transfer function?



$$Y(z) = V_2(z)[K_1 + (K_1K_2 + K_2)z^{-1} + z^{-2}]$$

$$X(z) = V_2(z)[1 + (K_2 + K_1K_2)z^{-1} + K_1z^{-2}]$$


$$\frac{Y(z)}{X(z)} = \frac{K_1 + (K_2 + K_1K_2)z^{-1} + z^{-2}}{1 + (K_2 + K_1K_2)z^{-1} + K_1z^{-2}} = \frac{z^{-2}A(z^{-1})}{A(z)}$$

**Question:** What kind of filter is this?

# Implementing Lattice Filters

## ■ Lattice Stage

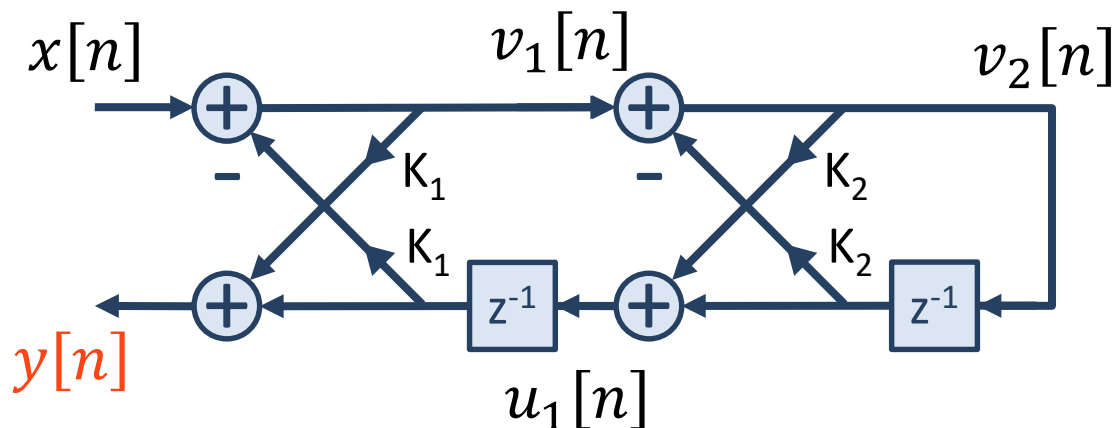- **Question:** What is the transfer function?



$$Y(z) = V_2(z)[K_1 + (K_1K_2 + K_2)z^{-1} + z^{-2}]$$

$$X(z) = V_2(z)[1 + (K_2 + K_1K_2)z^{-1} + K_1z^{-2}]$$


$$\frac{Y(z)}{X(z)} = \frac{K_1 + (K_2 + K_1K_2)z^{-1} + z^{-2}}{1 + (K_2 + K_1K_2)z^{-1} + K_1z^{-2}} = \frac{z^{-2}A(z^{-1})}{A(z)}$$

**Question:** What kind of filter is this? **All-Pass Filter**

# Implementing Lattice Filters

## ■ Lattice Stage

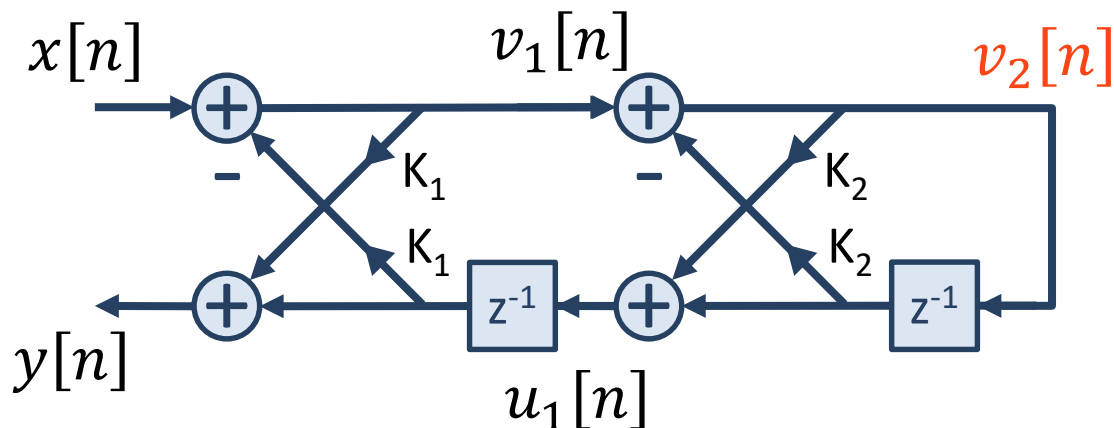- **Question:** What is the transfer function?



$$Y(z) = V_2(z)[K_1 + (K_1K_2 + K_2)z^{-1} + z^{-2}]$$


$$X(z) = V_2(z)[1 + (K_2 + K_1K_2)z^{-1} + K_1z^{-2}]$$

$$\frac{V_2(z)}{X(z)} = ?$$

# Implementing Lattice Filters

## ■ Lattice Stage

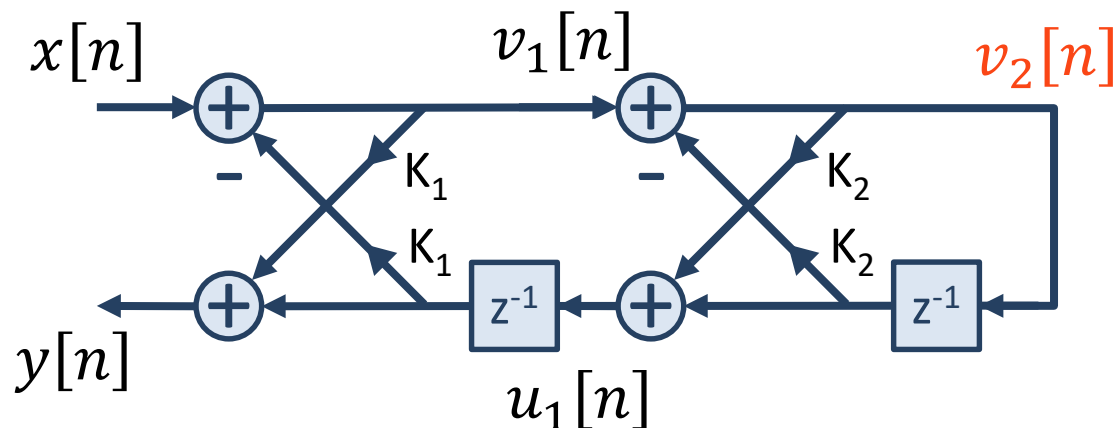- **Question:** What is the transfer function?



$$Y(z) = V_2(z)[K_1 + (K_1K_2 + K_2)z^{-1} + z^{-2}]$$

$$X(z) = V_2(z)[1 + (K_2 + K_1K_2)z^{-1} + K_1z^{-2}]$$


$$\frac{V_2(z)}{X(z)} = \frac{1}{K_1 + (K_1K_2 + K_2)z^{-1} + z^{-2}}$$

**Question:** What kind of filter is this?

# Implementing Lattice Filters

## ■ Lattice Stage

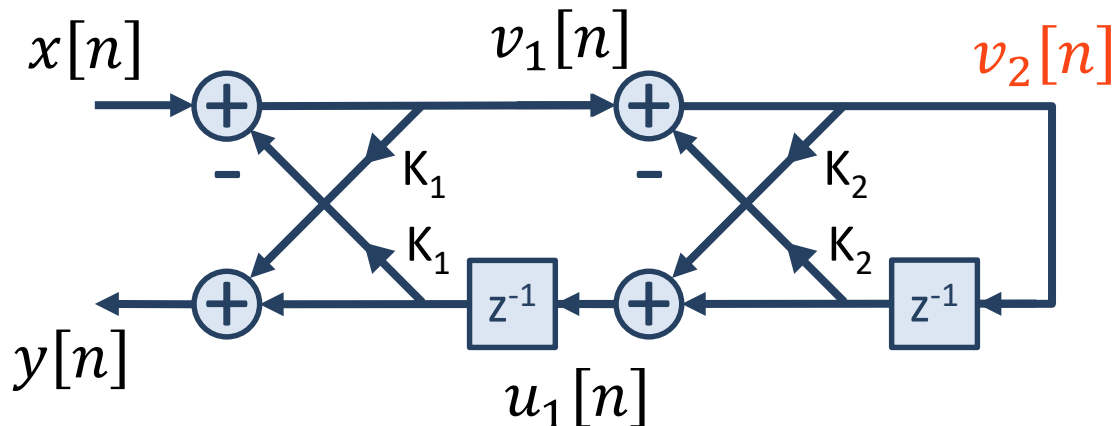- **Question:** What is the transfer function?



$$Y(z) = V_2(z)[K_1 + (K_1K_2 + K_2)z^{-1} + z^{-2}]$$

$$X(z) = V_2(z)[1 + (K_2 + K_1K_2)z^{-1} + K_1z^{-2}]$$

$$\frac{V_2(z)}{X(z)} = \frac{1}{K_1 + (K_1K_2 + K_2)z^{-1} + z^{-2}}$$


**Question:** What kind of filter is this? **IIR Filter**



# Implementing Lattice Filters

## ■ Lattice Stage

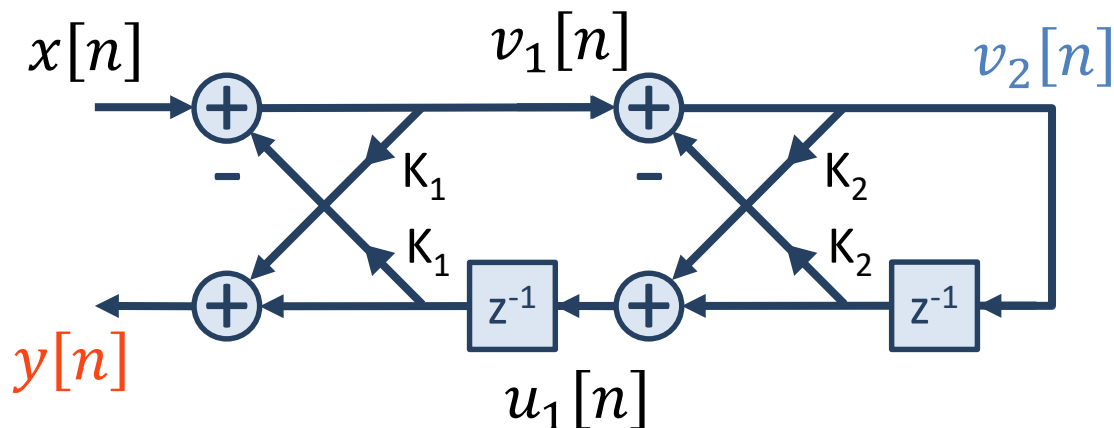- **Question:** What is the transfer function?



$$Y(z) = V_2(z)[K_1 + (K_1K_2 + K_2)z^{-1} + z^{-2}]$$


$$X(z) = V_2(z)[1 + (K_2 + K_1K_2)z^{-1} + K_1z^{-2}]$$

$$\frac{Y(z)}{V_2(z)} = ?$$

# Implementing Lattice Filters

## ■ Lattice Stage

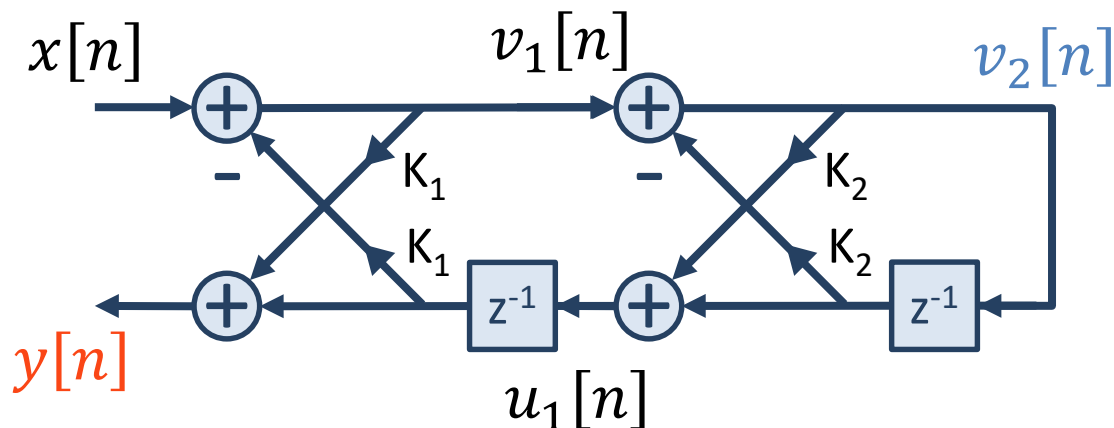- **Question:** What is the transfer function?



$$Y(z) = V_2(z)[K_1 + (K_1K_2 + K_2)z^{-1} + z^{-2}]$$

$$X(z) = V_2(z)[1 + (K_2 + K_1K_2)z^{-1} + K_1z^{-2}]$$


$$\frac{Y(z)}{V_2(z)} = K_1 + (K_1K_2 + K_2)z^{-1} + z^{-2}$$

**Question:** What kind of filter is this?

# Implementing Lattice Filters

## ■ Lattice Stage

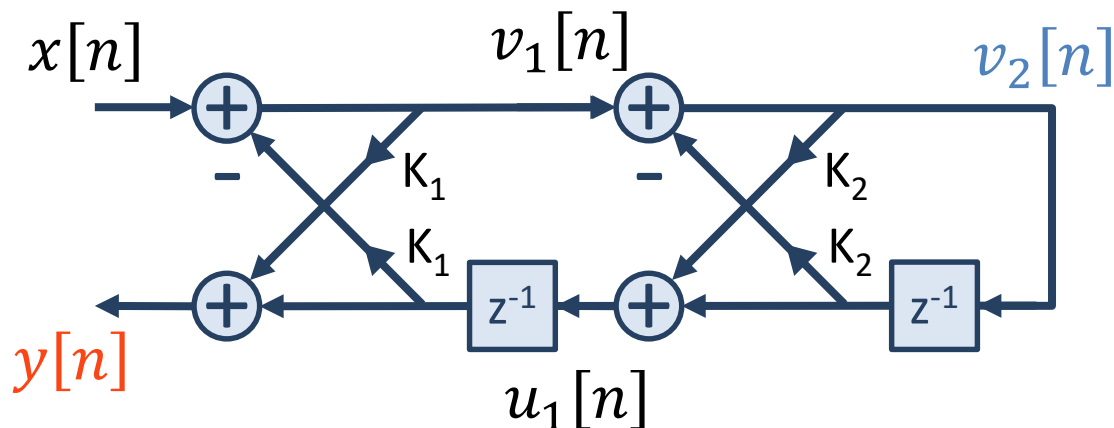- **Question:** What is the transfer function?



$$Y(z) = V_2(z)[K_1 + (K_1K_2 + K_2)z^{-1} + z^{-2}]$$


$$X(z) = V_2(z)[1 + (K_2 + K_1K_2)z^{-1} + K_1z^{-2}]$$

$$\frac{Y(z)}{V_2(z)} = K_1 + (K_1K_2 + K_2)z^{-1} + z^{-2}$$

**Question:** What kind of filter is this? **FIR Filter**

# Implementing Lattice Filters


## ■ Lattice Stage

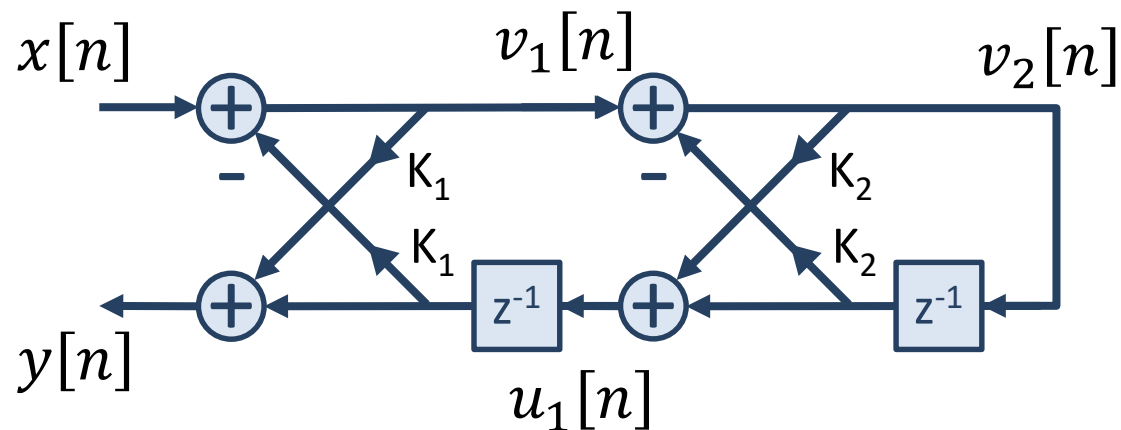

# Implementing Lattice Filters

## ■ Lattice Stage


### ■ All-Pass Filter

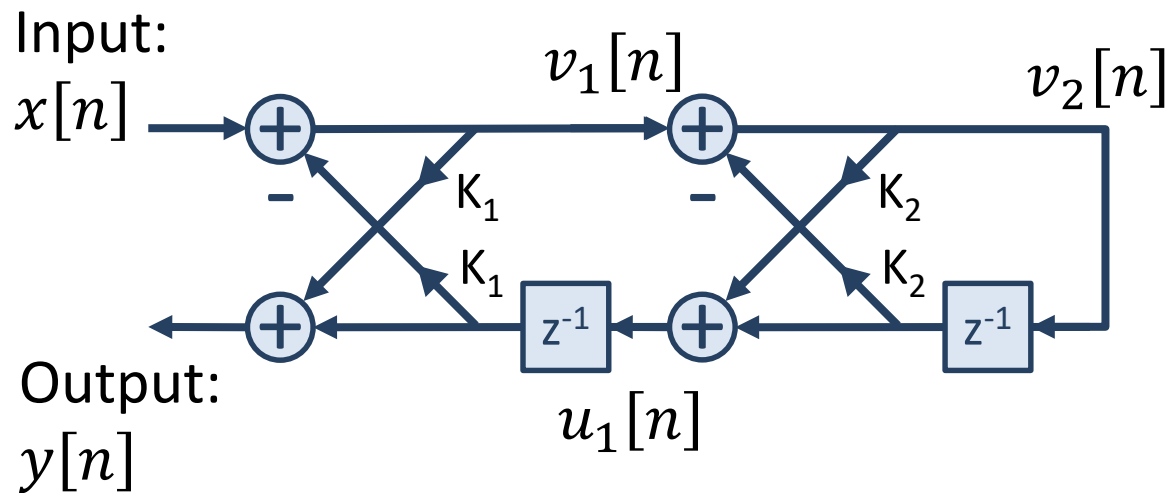

# Implementing Lattice Filters

## ■ Lattice Stage


### ■ IIR Filter

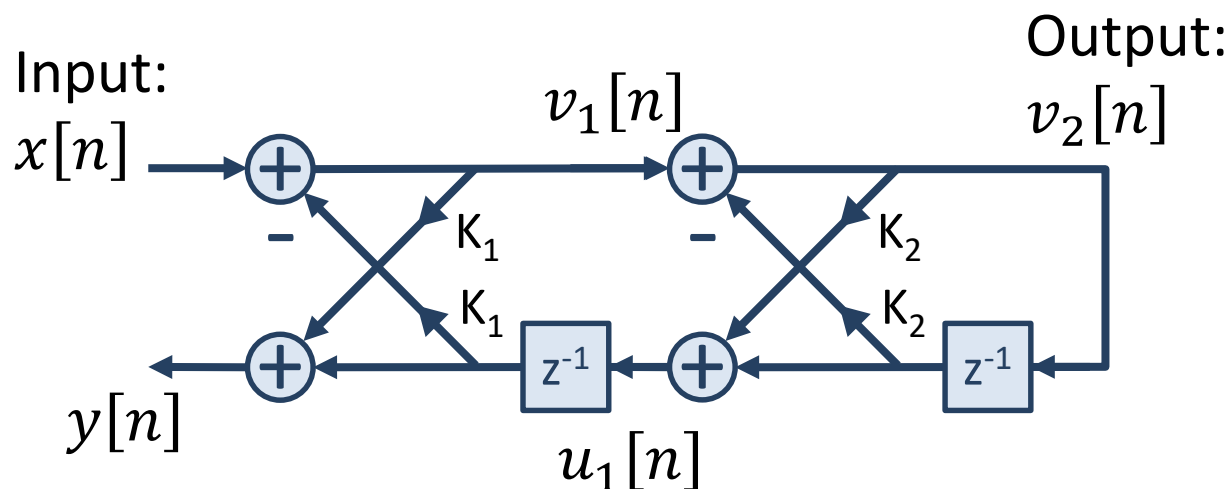

# Implementing Lattice Filters

## ■ Lattice Stage


### ■ FIR Filter

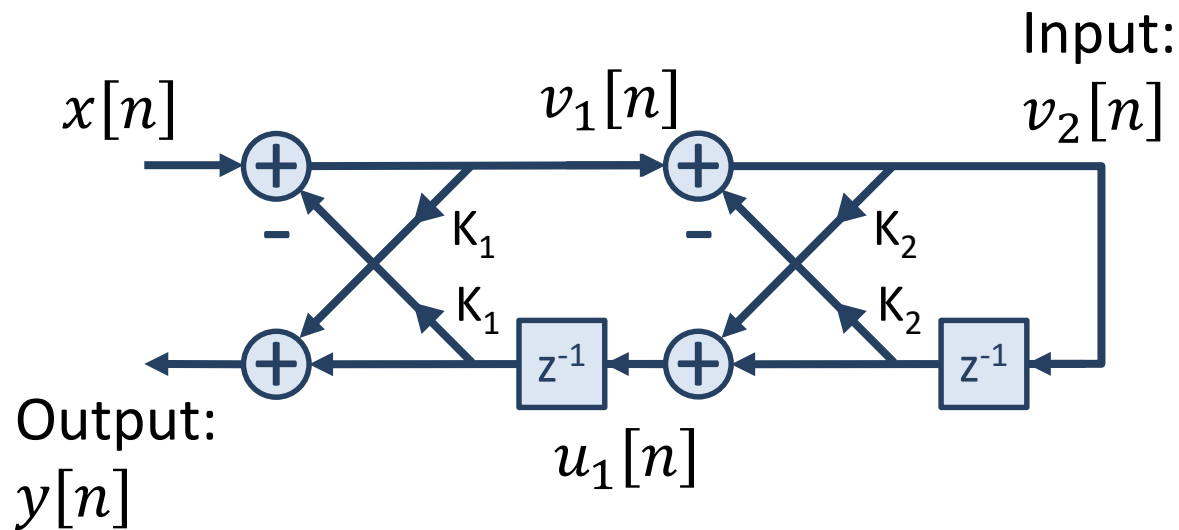

# Implementing Lattice Filters

## ■ Lattice Stage

### ■ Example:

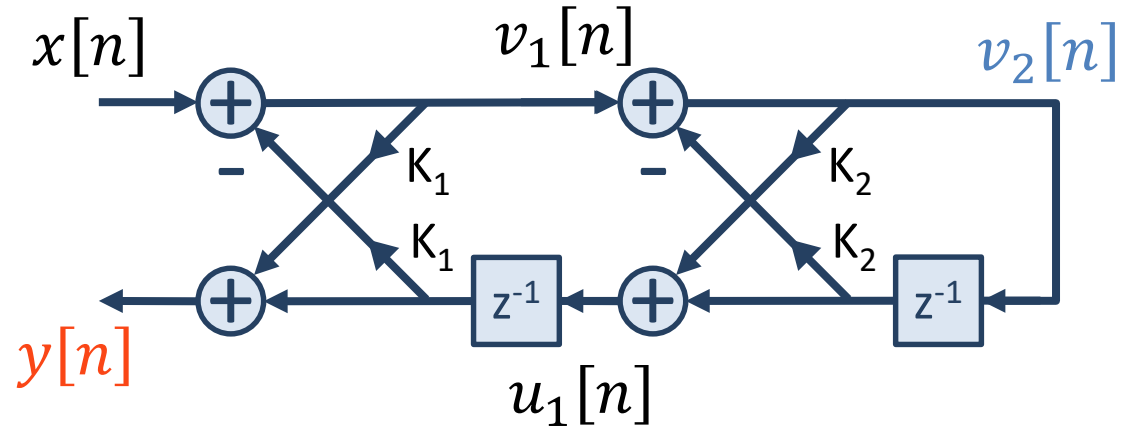



# Example

■ **Example:** Sketch the direct form II, parallel form, and cascade form for the system.

- $$y[n] = \frac{1}{4}y[n-2] + x[n]$$